


(4)

Unit - I

Electronics - I

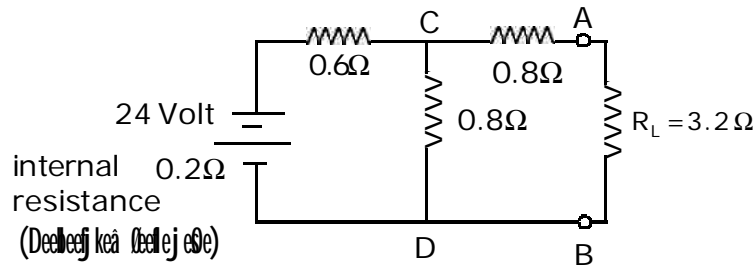
2. (a) State and prove Norton's theorem. Draw Norton's equivalent circuit of the following circuit. Calculate the current in the load resistance R_L . 6

ਵੇਖੋ ਅਤੇ ਇਸ ਦੇ ਨਿਰਧਾਰਣ ਕਰੋ। ਇਸ ਦੇ ਨਿਰਧਾਰਣ ਕਰੋ ਅਤੇ ਇਸ ਦੇ ਨਿਰਧਾਰਣ ਕਰੋ।
 ਹੇਠਲੇ ਦਿੱਤੇ ਸਰਕਟ ਦਾ ਨੋਰਟਨ ਦਾ ਸਮਾਨਾਨੁਕੂਲ ਸਰਕਟ ਡਰਾਓ।
 ਡਰਾਓ ਅਤੇ R_L ਵਿੱਚੋਂ ਲੰਘਣ ਵਾਲੇ ਕਰੰਟ ਦੀ ਗਣਨਾ ਕਰੋ।



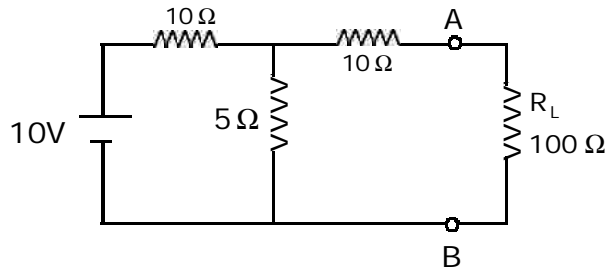- (b) Using Thevenin's theorem calculate current in the load resistance R_L in the following circuit. 5

ਲੇਵੇਂ ਦਿੱਤੇ ਸਰਕਟ ਵਿੱਚ ਡਿਊਨੀਥੈਨਿਨ ਦੇ ਥੈਨਮ ਦੀ ਵਰਤੋਂ ਕਰਕੇ ਲੋਡ ਵਿੱਚੋਂ ਲੰਘਣ ਵਾਲੇ ਕਰੰਟ ਦੀ ਗਣਨਾ ਕਰੋ।



S-609

A

(Printed Pages 8)

Roll No. _____

S-609

B.Sc. (Part-III) Examination, 2015

(Regular & Exempted)

PHYSICS

Third Paper

(Electronics)

Time Allowed : Three Hours]

[Maximum Marks : 75

Note : Answer five questions in all, including Question No. 1, which is compulsory and one question from each of the Units I, II, III and IV.

ਕੁਝ ਹੋਰ ਡਿਊਨੀਥੈਨਿਨ ਦੇ ਥੈਨਮ ਦੀ ਵਰਤੋਂ ਕਰਕੇ ਲੋਡ ਵਿੱਚੋਂ ਲੰਘਣ ਵਾਲੇ ਕਰੰਟ ਦੀ ਗਣਨਾ ਕਰੋ।

1. Answer each of the following questions:

ਉੱਚ ਦਿੱਤੇ ਸਰਕਟ ਵਿੱਚ ਡਿਊਨੀਥੈਨਿਨ ਦੇ ਥੈਨਮ ਦੀ ਵਰਤੋਂ ਕਰਕੇ ਲੋਡ ਵਿੱਚੋਂ ਲੰਘਣ ਵਾਲੇ ਕਰੰਟ ਦੀ ਗਣਨਾ ਕਰੋ : $3 \times 10 = 30$

- (i) Explain Thevenin's network theorem.

ਲੇਵੇਂ ਦਿੱਤੇ ਸਰਕਟ ਵਿੱਚ ਡਿਊਨੀਥੈਨਿਨ ਦੇ ਥੈਨਮ ਦੀ ਵਰਤੋਂ ਕਰਕੇ ਲੋਡ ਵਿੱਚੋਂ ਲੰਘਣ ਵਾਲੇ ਕਰੰਟ ਦੀ ਗਣਨਾ ਕਰੋ।

P.T.O.

(8)

Techeedle jveDeleskeleee netee nP Deeeej Deefveeele GImeUekea
hegeYe& Ce kaer JueeKuee keaapeS leLee Fmekea mLeeUelJe
iegeceka kaer ieCeevee keaapeS-

Unit - IV
FkaeF&- IV

8. Draw Drain characteristics and Transfer characteristics curves of JFET. Explain why drain current becomes constant in the Saturation region. Define parameters of FET. Establish a relation among them. 11
- metDe #eSe DeYeje Šapemšj ka dfekeameer Deefveee#eeCeka leLee
DevUeeUe Deefveee#eeCeka Je eaelkaesDeej sKele keaapeS leLee meePeefUe
ekea dfelele Deje melhele #eSe cellvelele kelcellmes peeler nP FET
ka DeUeeellkaes hej Yeelele keaapeS SJeGveka yeele cellmeyerDe
mLeehele keaapeS-
9. Write short notes on the following :
- (i) Zener diode as Voltage Regulator 3 ½
 - (ii) Silicon controlled Rectifier as a switch 3 ½
 - (iii) MOSFET 4
- dfeveeUeeKele hej met#ehle ešheCeer dfeekES -
- (i) pesej [eUee] Jeesišlee dfeUeeeka kaer lej n
 - (ii) dfeUeeeka keavšau [e° keajer Skeā emUe keer lej n
 - (iii) ceemhaš

(5)

3. (a) Design a low pass constant K filter for 600 ohm line to pass speech frequencies upto 2500CIS employing 5
- (i) T - Section
 - (ii) π - Section
- dfeveeUeeKele Dekeaj ka ehašj Jeie&DeUee ka jlesnš 600
Deese ueefvee ka dfeS Skeā dfevee heeme dfeUe K ehašj kaer
j Ueevee keaapeS epemekeer DeefveeUeeKaes iempoj veskaer GÜUelce
meece 2500CIS n
- (i) T - Jeiel
 - (ii) π - Jeiel
- (b) Derive an expression for the width of depletion layer in a pn junction diode. Discuss how the depletion layer width depends on the concentration of impurity. 6

Ska pn metDe [eUee] ka dfeS Dele#eUe helerka JÜepe kaer
JÜeUee keaapeS- JÜeeKuee keaapeS eka Dele#eUe helerkaer
UeeUeF&eKaame Dekeaj Dellegee melveleee hej dfeUe keaj leer nP

Unit - II
FkaeF&- II

4. (a) What are Thermistors? Discuss their characteristics and give some of their applications. 5
- Techeedle DelejeSe keleee netee nP Fveka Deefveee#eeCeeUee
JÜeeKuee keaapeS leLee Fveka GheUeeellkae GuueKe keaapeS-

(6)

- (b) Give definition of four hybrid parameters. Draw hybrid parameter equivalent circuit of an amplifier in common base, common emitter and common collector configurations. 6

Ueej (kkaej ka mekaej le Deueellkaes heej Yeekete kaapeS-
 ekaameer DeJekka ka mekaej le Deuee legUe heej heLe GYeJee%
 DeDeej eDee, GYeJee% GImepka eDee leLe GYeJee%
 mekeener eDee cellKeeUeS-

- 5. (a) What are Tunnel Diodes? Draw their characteristic curve what are their applications? 5

mejhe [eJee] kahee nes nP Fveka DeJee#eCeka Jeka
 KeeUeS leLe Fveka GheJeeellkae GuueKe kaapeS-

- (b) Derive the expression of concentration of electrons and holes in intrinsic semiconductors. Find out the position of Fermi level in the forbidden energy gap in intrinsic semiconductor. Show it in the energy band diagram. 6

Mege DeDeueeka cellFuekeS leLe eDeJeeellkae meDee kee
 JUpka eDeeetele kaer
 kaer enLeelle Jeepele Tpee&DeJeeue cell%eele kaapeS leLe
 Tpee&yeQ Deej Ke cellOmeeFUs-

(7)

Unit - III
FkaeF- III

- 6. (a) Describe instability of θ -point and need of transistor biasing circuits. Describe Potential Divider biasing and derive the expression of its stability factor. 6

θ -efvogDeemLej le leLe ŠePmŠj DeJeeete heej heLe kaer
 DeJemUekaLee kaer JueKUee kaapeS- eDeYeJe eJ epeka
 DeJeeete kaer JueKUee kaapeS leLe Fmeka mLeedJee
 iefceka kaer JueJeebe kaapeS-

- (b) What are the main advantages of negative feed back amplifier. Prove mathematically that band width of an amplifier increases by the application of negative feed back. 6

Se+Ceelceka heyeYeCe ka celUe ueYe kahee nP eeCelee
 ehe cellweeze kaapeS eka Se+Ceelceka heyeYeCe DeJee
 kaJveshej DeJekka kaer yeQ [UeeF&yeQ peeteer nW

- 7. (a) Discuss the characteristics of class B Power amplifier. Calculate its efficiency. Describe Push-Pull class B amplifier. 6

Jeie&B meebe DeJekka ka DeJee#eCeellkaer JueKUee kaapeS-
 Jeie&B ka-eekeka-ee DeJekka kaer Jeeete kaapeS-

- (b) What is Thermal Runaway? Describe Base bias with emitter feed back method of biasing. Derive the expression of its Stability Factor. 6