

(4)

keâ keâeSofSJe, SmeesmeSesJe leLee ofmšâUofSJe ofreUeeel
keâe DekeâLeve keâeS leLee Fvns ofmeze keâeS-

(b) Simplify the Boolean expressions:

yeUeeUeUe JUepkeâeWkeâes mejue keâeS:

(i) $A + \overline{B}C$ ($A + \overline{BC}$)

(ii) $(A + \overline{A}B)(A+B)(\overline{A} + \overline{B})$

7. Reduce using K-Maps and implement in NAND or NOR logic:

K-eme keâe DeUeeie keâj les nš meceveUeUe keâeS SJeB NAND
DeLee NOR lekeâ ceUueeiet keâeS-

(i) $Y = \sum m(0, 1, 5, 8, 9, 10, 12, 13, 14)$

(ii) $Y = \sum T(1, 2, 3, 7)$

(iii) $Y = \sum m(1, 2, 3, 4, 9, 10, 11, 12)$

(iv) $Y = \sum T(1, 3, 5, 7, 9, 11, 13, 15)$

Unit-IV / FkeâF-IV 7½

8. Explain The working of a multimeter by a labelled diagram.

ceUŠer ceUŠj keâer keâeUeeCeeuer keâes Skeâ mejUeeemLele jKeedUeŠe
Éeje mecePeeFS-

9. Explain the principle and construction of a cathode ray oscilloscope. Draw a well-labelled diagram for the same.

keâLees[js Deemueemkeâe keâe ofmezevle SJeB âeUeeCeeuer keâe
mecePeeFS- Gmekeâe mejUeeemLele jKeedUeŠe Yeer yeveeFÙes

A

(Printed Pages 4)

Roll No. _____

S-611

B.Sc. (Part-I) Examination, 2015

ELECTRONICS

Second Paper

Time Allowed : Three Hours] [Maximum Marks : 50

Note : Answer five questions in all Question No. 1 is compulsory. Attempt one question from each Unit.

keâue heeÙe DeUveeUkeâe Goej oeepeS- DeUve meb1 DeUeeUeeUerw
DeUeeUeâ FkeâF&mes Skeâ DeUve keâeS-

1. Answer all the following : $2 \times 10 = 20$
ofrecveUeeKele meYeer keâe Goej oeepeS :

(i) Define Gray Code

«es keâe[heej Yeekete keâeS-

(ii) Convert decimal number 1426.25 to binary number.

[ofmeceUe Dekeâ 1426.25 keâesyeefvej er Dekeâ ceUheej Jeel ete
keâeS-

(iii) Define Minterm.

ofevšce& keâes heej Yeekete keâeS-

(2)

(iv) Convert octal number 257 to decimal number

Deekāśue Dekeā 257 kās [omeceue Dekeā celheej Jeeleke kēāpēs~

(v) Explain seven segment decoder

meceve meiceceś e[keās]j kās mecePeeFS~

(vi) Draw the logic circuit diagram of

$$y = (A+B) \cdot \bar{C}$$

$$y = (A+B) \cdot \bar{C} \quad \text{kāe lēkē heej heLe yeveeFS~}$$

(vii) Define Parity

heej Šer kās heej Yeekele kēāpēs

(viii) What is power supply?

heej mehuceF&kālee neeer nP

(ix) Give two application of a C.R.O

meer Deej .Dees kā oes GheUeeie oepēs~

(x) What is synchronization?

ehev>āesveFpebleve kālee neee nP

Unit-I / FkēāF-I 7½

2. Explain why binary numbers are used in logic circuit. Describe the method of converting from binary to decimal and decimal to binary.

mecePeeFūs ekeā lēkē heej heLeell/cell/yeefvej er Dekeāll/kāe DeUeeie kālee ekeālee peete nP yeefvej er mes [omeceue SJeB [omeceue mesyeefvej er cel heej Jeeleke kēā ves kāer eleeDe kās Jeeleke kēāpēs~

3. What are weighted BCD codes and non-weighted codes? Discuss in details sequential and reflective codes.

(3)

Jēs [yeer meer [er kās [the leLee veeve Jēs [kās [me kālee nees nP
emekeesMeUee SJeB j heeskeās Je kās [ellkēer e[em]eLe UeUee&kēāpēs~

Unit-II / FkēāF-II 7½

4. What is OR gate? Discuss its logic operation write truth table for three input OR gate. Design OR gate using diodes. Explain the difference between OR gate and AND gate.

OR iēs kālee neee nP Fmekeā lēkē Dehej Meve kāer UeUee&kēāpēs~
leere Fveheś OR iēs kāer melUeeve mee Ceer eleeKēs- [eUee [the
kāe DeUeeie kāj OR iēs kāer j Uevee kēāpēs- OR iēs SJeB AND
iēs celDevlej mecePeeFS~

5. (a) What is the difference between XOR and XNOR gate? Explain the operation of XNOR gate with the help of its logic circuit.

XOR SJeB XNOR iēs ellcelDevlej kālee nees nP XNOR
iēs kāe DeUeeve Gmekeā lēkē heej heLe kāer meneUee me
mecePeeFS~

(b) Explain the operation of NAND gate and show that it is a Universal gate.

NAND iēs kāe DeUeeve mecePeeFS Deej Uen oMeef Ues ekeā
NAND iēs kāe meelekeā iēs nP

Unit-III / FkēāF-III 7½

6. (a) State and prove the Commutative, associative and distributive laws of Boolean Algebra with logic design.

ueep ekeā e[peefve kāe GheUeeie kāj les nP yetUeeve Sūpeyej e