

(4)

5. Define CMRR. Establish an expression for CMRR in a difference amplifier.

CMRR keās heif Yeekele keāspējell Skeā Yes deJeokēa cell CMRR
keā eueJēs Jūspēkēa mLeefele keāspējles

Unit-III / FkeāF-III

7½

6. Discuss the principles of feedback. Describe the advantages of negative feedback in detail.

hegeYej Ce keā emeEelle keār ejeJēsvee keāspējles \$eCeelceka hegeYej Ce
keā ueeYeb keār ejeJēsvee JūekKūe keāspējles

7. Discuss the step response of an amplifier.

Skeā deJeokēa keā heo DevefēaLee keār ejeJēsvee keāspējles

Unit-IV / FkeāF-IV

7½

8. Draw the circuit diagram of a voltage series feedback for CE amplifier and give the mathematical analysis of its various parameters.

Skeā CE deJeokēa nsejJesjLee BeCeer hegeYej Ce keā
yeveeFüesleLee Gmekeā ejeJēsvee deJeokēa keār
mecetee keāspējles

9. Draw the circuit diagram of a class A audio power amplifier and calculate its maximum collector efficiency.

Skeā Jeie& A deKeaj keā BeJUe Meefēa deJeokēa keār heif heLē
yeveeFües Deej Gmekeā eueJēs DeJeokēa ce mekeener o#elee keār ieCevee
keāspējles

A

(Printed Pages 4)

Roll No. _____

S-612

B.Sc.(Part-I) Examination, 2015

ELECTRONICS

Paper - III

(Amplifiers)

Time Allowed : Three Hours] [Maximum Marks : 50

Note : Answer five questions in all. Question No. 1 is compulsory. Attempt one question from each Unit.

keāg heejle deMveekēa Gōej oepēs~ deMve meb 1 DeefjeJēnW
deJUekēa FkeāF&mes Skeā deMve keāspēs~

1. Write short answers of the following:

2x10 =20

- Define thermal runaway.
- Explain briefly the load line.
- Write the advantages of using h-parameter model.
- Why is the negative feedback applied in high gain amplifiers ?

(2)

- (v) What are the characteristics of a good difference amplifier ?

(vi) What are the woofer and tweeter? Draw the circuit diagrams of the following.

(vii) A Common source FET amplifier.

(viii) CC-CE configuration

(ix) CE- CB configuration

(x) A current shunt feedback amplifier.

(i) Tæcetle heuedjeve keæs heej Yeekele keæspelles

(ii) Yeej j Kee keæs meñele cellmecePeeFües

(iii) h- ñeñue cee[ue keæs Gheñue keaj ves kei ueeYe eñeñKeñes

(iv) GUe ueeYe ñeñoleka cell \$+Ceñlcekeá heyeYej Ce keñlellueieñee
peelæ nw?

(v) Skeâ Göece Yes ñeñoleka keâ keñlee ueñeCe netes nP

(vi) Jheaj Deejj ſdeñsj keñlee netes nQ?
eñeñeñeñKele keâ heej heLe eñeñe yeveeFües

(vii) Skeâ GYeñueñe%o ceñe FET ñeñoleka

(viii) CC-CE eñeñueeme

(ix) CE-CB eñeñueeme

(X) Skeâ Oeej e Melj heyeYej Ce ñeñoleka

(3)

Unit-I / FkææF-1

7½

2. Draw the circuit diagram of a common collector amplifier using hybrid parameters and derive the expressions for current gain, voltage gain, input resistance and output, resistance ?

neFefejf leelueueWkeæs leeluee keaj les ngs, Skeá GYleefre‰o meleenele leleleka keæ heej hele eñlese yeveefUes leLee Oeej e ueeYe, Jeœšllee ueeYe, eñlelele leel ej eñle leel ej eñle keä eñleles JUlepekeä eñlekeæeñleles

3. discuss the cause for bias instability in a transistor. Describe the methods of transistor biasing in short Prove that self bias is the best biasing method.

Skeá Šepemšj cellyeeüeme DeemLej lee keä keaj CeeWkeäer JUeeKUee keajpeljW Šepemšj yeeüefnelie keäer eñleDeuelWkeæs melelece celJeeCee keajpeljW eñeaæ keajpeljles keäer mje yeeüeme melelece yeeüefnelie eñleDeuelW

Unit-II / FkeafF-II 7½

4. Draw a circuit diagram of a common drain FET amplifier and find out the expressions for voltage gain, input and output resistances.

Unit-II / FkææF-III

7½

4. Draw a circuit diagram of a common drain FET amplifier and find out the expressions for voltage gain, input and output resistances.