

A

(Printed Pages 7)

Roll No. _____

S-617

B.Sc. (Part III) Examination, 2015

ELECTRONICS

Second Paper

(Linear Electronics)

Time Allowed : Three Hours] [Maximum Marks : 75

Note : Answer five questions in all. Question No.1 is compulsory. Attempt one question from each unit.

keq ue heeBe ðelMveellkeá Gøej oeepeS- ðelMve meB 1 DeereJeeÙe&nw
ðelÙekeá FkeáeF&mes Skeá ðelMve keáeepeS-

1. Write short answer of the following :

erecveeÙeekEle keá meB#ehle Gøej erecKeeÙes $3 \times 10 = 30$

(i) Define input offset voltage and input offset current of an op-Amp.

Skeá op-Amp keá ereJeeÙe Deekáameš Jeeššpe SJeB ereJeeÙe
Deekáameš Oeeje keáes heej YeeekEle keáeeÙe

P.T.O.

(2)

- (ii) What is common mode rejection ratio?
Explain its importance.

GYeUeure%o eDeOee efrej ekeaj Ce Devegeele keblee nif cenIJe
keaes mecePeeFÜes

- (iii) Explain the parameters that should be considered for ac and dc application of an op-amp.

Skaä op-Amp kaä S.meer. SJeB [er.meer. DevegeÜeesie kaä
eDeÜes eDeÜeej eLe& ceheoÜes kaäs mecePeeFÜes

- (iv) What is thermal drift? How does it affect the performance of an op-Amp?

G-ceede yenele keblee nif Üen op-Amp kaä ÖeoMette keäer
keimes ÖeYeeDele keaj lee nif

- (v) Explain the limitations of open loop op-Amp configuration.

op-Amp kaä Kegesude Dekeaj keärmeceeeDeelkeäsmec eeFÜes

- (vi) Differentiate between active and passive filters.

meDeaÜe eDeäuŠj SJeB efrekcaÜe eDeäuŠj ceWDeVlej mhe°
keäefj Ües

(7)

put voltage. If a square wave is applied to the input of differentiator sketch the output waveform.

DeJekeäuekeä keblee nif GheÜgeä heefj heLe DeejKe Éeje op-Amp
DeJekeäuekeä keäer keäeÜeDe mecePeeFÜesDeejj Fmekeä yeehJemmeer JeesiŠpe
kaä eDeÜes yÜepkeä Öehte keäefj Ües Üeeb DeJekeäuekeä kaä eDeJemmeer hej
mkeäeÜej lejlie kaäs Deejoshele ekeäÜee paeÜe lees Fmekeä yeehJemmeer
lejlie kaäs DeejosKele keäefj Ües

9. What is the function of voltage regulator? Discuss the various factors to determine the quality of regulated power supply. Draw the block diagram of a regulated power supply and explain its working.

JeesiŠpe eDeÜeecekeä keäe keblee keäeÜe&nif Skaä eDeÜeecele eDeÄeje Öeoehe
keäer iefjeÜee eDeÜeej Ce keaj ves kaä eDeÜes eDeeÜe keaj kaäs hej ÜeÜee
keäefj Ües Skaä eDeÜeecele eDeÄeje Öeoehe kaä yeekeä DeejKe KeDekeaj
Fmekeä keäeÜeCeeueer keäer mecePeeFÜes

(4)

keā mecelegū he hē kēdēdesDeej Gmekā JeesŠpe nmlēvleJCe
Jevā keās mecePeeFŪes

- (b) Draw the circuit diagram of an ideal op-Amp based non investing amplifier and explain the expression for voltage gain.


Skeā DeoMēk op-Amp DeoDeej le igj FveJeeŠte ņeJeOkeā
keā he hē Deej Ke KeāņeS SJeG Gmekā ye h Jēleer yeēSŠle
keā JŪepēkeā ņe hē keāņ Ūes

- 3. (a) The differential input op-Amp shown in fig.1 consists of a base amplifier of infinite gain. Show that

$$V_{out} = \frac{R_2}{R_1} (v_2 - v_1)$$

ēDeSe 1 celņoēMēte ēleYeēer ēreJeMēer op-Amp Devele ueYe
keā Skeā DeoDeej ņeJeOkeā meēēvekeāj yeve nņ ēkeā
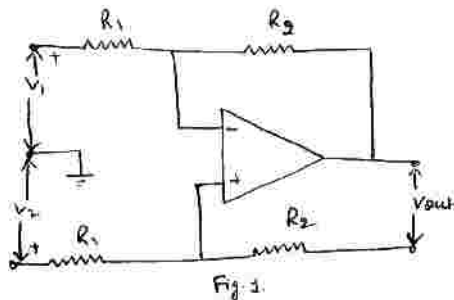
$$V_{out} = \frac{R_2}{R_1} (v_2 - v_1)$$



(5)

- (b) Draw the schematic diagram of an 741 op-Amp IC and describe function of each pin.

op-Amp IC 741 keā Ūeēpeveēyeēe Deej Ke Keāņeņe
Deej Fmekā ņelŪekā ēheve keā keāņeēkeā JeCēte keāņ Ūes

Unit-II / FkeāF-III 11

- 4. Define slew rate and explain its causes. Determine the full power bandwidth of the 741 op-Amp with Vin=supply voltage = 15 v, consider slew rate for 741 op-Amp is 0.8v/μ sec.

ōJe leCēte keās he hē Yeēēle keāņ Ūes Deej Gmekā keāj Ceēkeāer JŪeKŪe
keāēpeŪes 741 op-Amp keā ōJe leCēte keās 0.8v/μ sec
cevele snņes Vin = me h ueēF & JeesŠpe = 15 v keā me le Ce&Mēbeā
Jeņēle ņe keā ēreDeej Ce keāņ Ūes

- 5. What is voltage follower? Explain the advantage of voltage follower amplifiers. Draw the circuit diagram of voltage follower and explain its working.

JeesŠpe Hāēueēēēj keŪee nņ? JeesŠpe Hāēueēēēj ņeJeOkeā keā ueYe
keāer JŪeKŪe keāēpeŪes Skeā JeesŠpe Hāēueēēēj keā he hē Deej Ke
KeāņeS SJeG Gmekāer keāņeēēēē keās mecePeeFŪes

(6)

Unit-III / FkæF-III

11

- 6. What is summing amplifier? Draw the circuit diagram of op-Amp based summing amplifier using non investing configuration and determine expression for output voltage.

Ùeepeer ðeJeOekæ keålee nî? iej FveJeeSîe Deekæej keæ Ghelleeie keåj Skeå op-Amp DeeOeeefj le Ùeepeer ðeJeOekæ keæ heefj heLe DeeJKe KeeðÙeS SJeB Fmekeå yeefnJeeMeer JeeSîlee keæ JÙelpokeå ðeehle keåefj Ùes

- 7. What is an instrumentation amplifier? How does it differ from ordinary amplifier? Draw the schematic diagram of an instrumentation amplifier and explain its working.

Ùelleekæej Ce ðeJeOekæ keålee nî? Ùen meeOeej Ce ðeJeOekæ meskeåmesDeueie nî? Ùelleekæej Ce ðeJeOekæ keæ Ùeepeveeyeeæ DeeJKe yeveekæej Fmekeå keåÙe& ðeCeeueer keåes meecePeeFÙes

Unit-IV / FkæF-IV

12

- 8. What is differentiator? Explain the working of on op-Amp differentiator with suitable circuit diagram and determine the expression for out-

(3)

- (vii) How we can improve the accuracy of dc amplifiers?

nce [er.meer. ðeJeOekæ keåer meŠkeålee ceb keåmes mefjeej keåj mekeåles nî?

- (viii) Explain the difference between positive scalar and voltage to current converter.

Oeveelcekeå mkeåuej SJeB yeesuŠpe mes Oeeje heefj Jelekeå keå Devlejj keåes meecePeeFÙes

- (ix) What are the limitations of linear voltage regulator?

jKeeble JeeSîŠpe ðreÙeecekeå keåer keålee meeceÙellnî?

- (x) Explain the resolution of a DAC.

Skeå [er.S.meer. keå mekeåuhe keåes meecePeeFÙes

Unit-I / FkæF-I

15

- 2. (a) What are the properties of an ideal op-Amp? Draw the equivalent circuit of an op-Amp and explain its voltage transfer curve.

Skeå DeeoMe&op-Amp keå keålee iefje nî? Skeå op-Amp