

Dr. R. K. SHUKLA.
Department of Physics.
University of Lucknow.

A/D and D/A Conversion.


Analog-to-Digital Conversion:- The process of changing an analog signal to an equivalent digital signal is accomplished by the use of an A/D Converter. For example, an A/D converter is used to change the analog output signals from transducers into equivalent digital signals. These signals would then be in a form suitable for entry into a digital system. An A/D converter (ADC) is often referred to as an encoding device since it is used to encode signals for entry into a digital system.

A number of different methods have been developed.

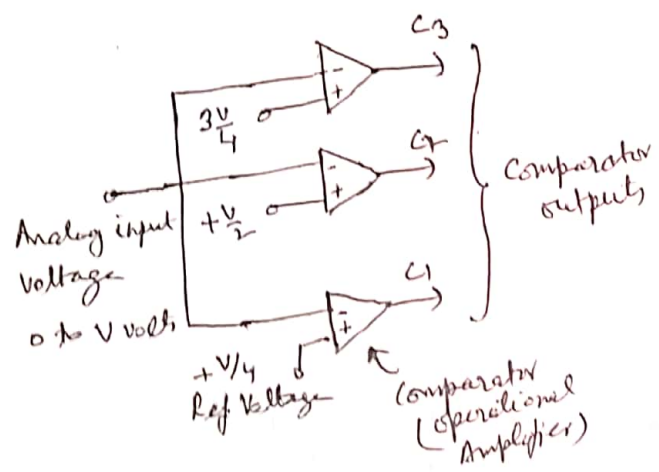- (1) Counter method
- (2) Simultaneous method
- (3) Continuous A/D conversion
- (4) Dual-slope A/D conversion

A/D Converter - simultaneous method:- The simultaneous method of A/D conversion is based on the use of a number of comparator circuits. The analog signal to be digitized serves as one of the inputs to each comparator. The second input is a standard voltage.

If the analog input signal exceeds the reference voltage to any comparator that comparator turns on. Now, if all the comparators are off, the analog input signal must be between 0 and $+V/4$. If C_1 is high (comparator C_1 is on) and C_2 and C_3 are low, the input must be between $+V/4$ and $V/2$. If C_1 and C_2 are high while C_3 are low, the input must be between $+V/2$ and $3V/4$. Finally, if all comparator outputs are high, the input signal must be between $+3V/4$ and $+V$. The comparator output levels for the various ranges of input voltages are summarized.




Input Voltage	Comparator output			Binary output	
	C_1	C_2	C_3	2^1	2^0
0 to $+V/4$	L	L	L	0	0
$+V/4$ to $V/2$	H	L	L	0	1
$+V/2$ to $3V/4$	H	H	L	1	0
$+3V/4$ to $+V$	H	H	H	1	1

Comparator outputs for input voltage ranges.


The reference voltages used are $+V/4$, $+V/2$ and $+3V/4$. The system is then capable of accepting an analog input voltage between 0 and $+V$.

For the 2-bit converter, there are three comparators were necessary for defining four ranges ($2^2=4$). In general, it can be said that 2^n-1 comparators are required to convert to a digital signal that has n bits. There are four voltage ranges that can be detected by this converter. Four ranges can be effectively discerned by two binary digits. The three comparator outputs can then be fed into a coding

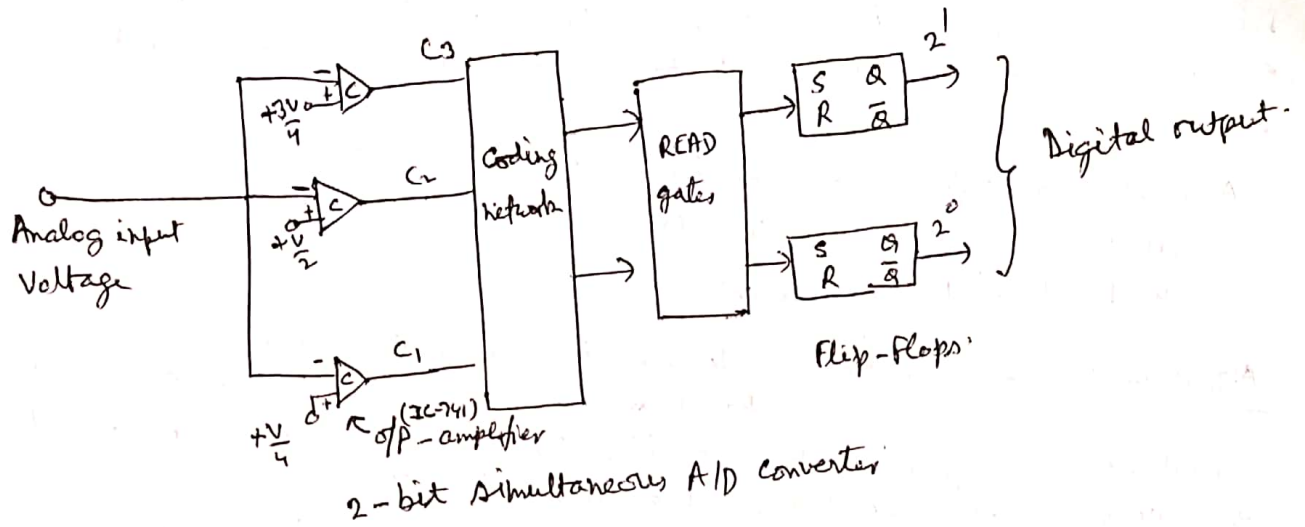
network to provide 2 bits which are equivalent to the input analog voltage. The bits of the coding network can then be entered into a flip-flop register for storage. The complete block diagram for such an A/D Converter is shown in below fig.



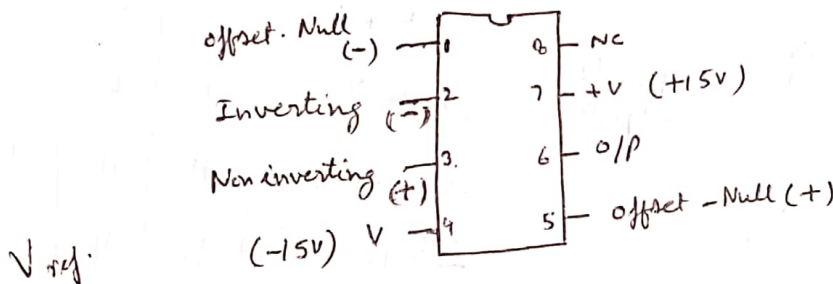Digital Principles and Applications
 Albert Paul Malvino & Donald P. Leach
 Tata Mc Graw-Hill Publishing Company Limited



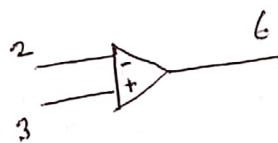
→ Difference amplifier
 two input $\begin{cases} \text{Inverting} \\ \text{non-inverting} \end{cases}$



~~A (inverting)~~ ~~A (non-inverting)~~
 $A(\text{non-inverting}) - B(\text{inverting})$
 = output (A-B)

To gain a clear understanding of the operation of the simultaneous A/D converter, let us investigate the 3-bit Converter shown in below figure. In order to convert the input signal to a digital signal having 3 bits, it is necessary to have seven comparators (this allows a division of the input into eight ranges).

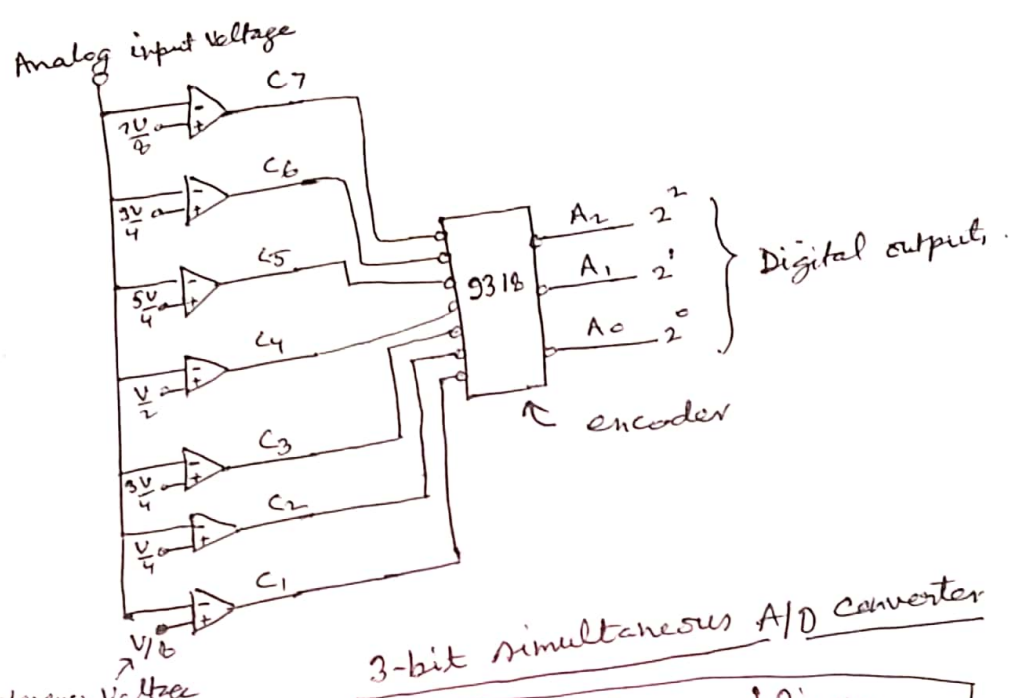The ~~enc~~ encoding matrix must accept seven input levels and encode them into a 3-bit binary number (having eight possible states). Operation of the encoding matrix can be most easily understood by examination of the table of outputs in figure.



3-bit simultaneous A/D converter

Input Voltage	Comparator for level							Binary output		
	C ₁	C ₂	C ₃	C ₄	C ₅	C ₆	C ₇	2 ²	2 ¹	2 ⁰
0 to V/8	L	L	L	L	L	L	L	0	0	0
V/8 to V/4	H							0	0	1
V/4 to 3V/8	H	H						0	1	1
3V/8 to V/2	H	H	H					1	0	0
V/2 to 5V/8	H	H	H	H				1	0	1
5V/8 to 3V/4	H	H	H	H	H			1	1	0
3V/4 to 7V/8	H	H	H	H	H	H		1	1	1
7V/8 to V	H	H	H	H	H	H	H	1	1	1

Logic table for the converter

Digital-to-Analog Converters :- Digital-to-analog (D/A) and analog-to-digital (A/D) conversion form two very important aspects of digital data processing. Digital-to-analog conversion involves translation of digital information into equivalent analog information. As an example, the output of a digital system might be changed to analog form for the purpose of driving a pen recorder.


Digital-to-analog conversion is a straight forwarded process and is considerably easier than A/D conversion. In fact, a D/A converter is usually an integral part of any A/D converter.

The digital word is presented in a variety of codes, the most common being pure binary or binary-coded-decimal (BCD).


The output V_o of an N -bit D/A converter is given by the following equation:

$$V_o = (a_{N-1}2^{-1} + a_{N-2}2^{-2} + a_{N-3}2^{-3} + \dots + a_02^{-N})V_R \quad \text{---(1)}$$

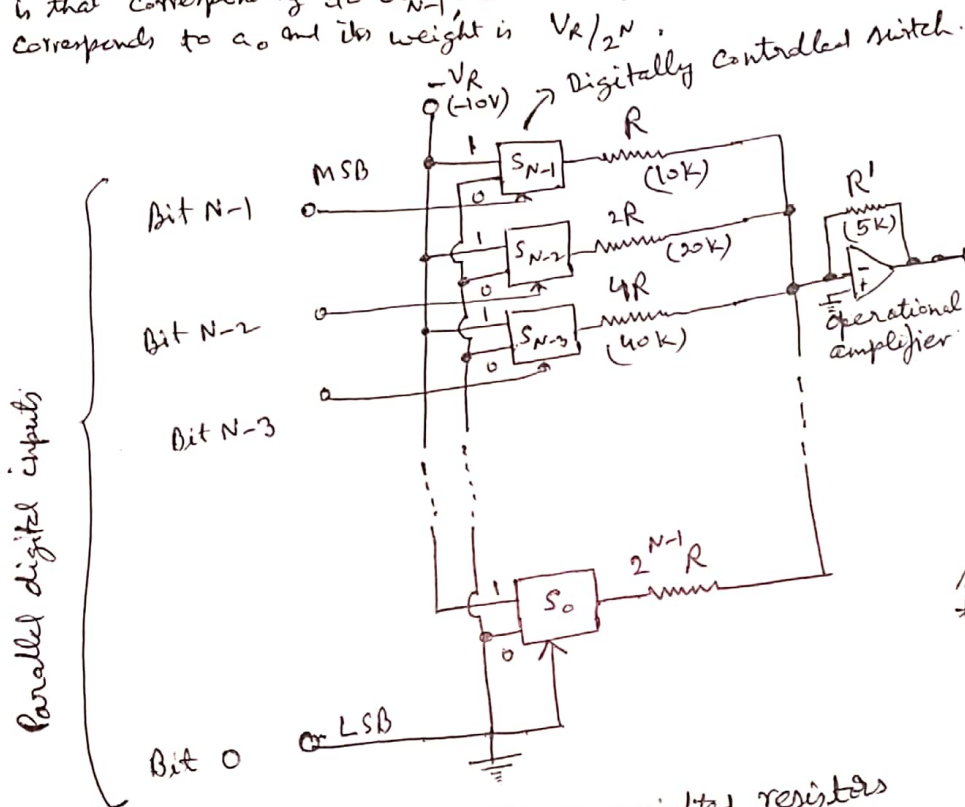where the coefficients a_n represent the binary word and $a_n = 1(0)$ if the n th bit is 1(0). The voltage V_R is a stable reference voltage used in the circuit. The most significant bit (MSB) is that corresponding to a_{N-1} and its weight is $V_R/2$, while the least significant bit (LSB) corresponds to a_0 and its weight is $V_R/2^N$.



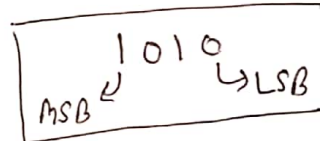The blocks $S_0, S_1, S_2, \dots, S_{N-1}$ are electronic switches which are digitally controlled. For example, when a 1 is present on the MSB line, switch S_{N-1} connects the 10-K resistor to the reference voltage $-V_R (-10V)$; conversely, when a 0 is present on the MSB line, switch connects the resistor to the ground line. Thus: switch is a single-pole double-throw (SPDT) electronic switch.



D/A Converter with binary weighted resistors

Consider, for example, a 5-bit word ($N=5$), so that Eq (1) becomes.

$$V_o = \left(\overset{\text{MSB}}{a_4} \frac{1}{2} + \frac{a_3}{4} + \frac{a_2}{8} + \frac{a_1}{16} + \underset{\text{LSB}}{\frac{a_0}{32}} \right) V_R$$

$$= \left(16a_4 + 8a_3 + 4a_2 + 2a_1 + a_0 \right) \frac{V_R}{32} \quad \text{---(2)}$$

For simplicity, assume $V_R = 32V$. Then, if $a_0 = 1$ and all other a_i are zero, i.e. $a_1 = a_2 = a_3 = a_4 = 0$, then eq (2) becomes

$$V_o = 1.$$

∴ If $a_1=1$ and all other a_i 's are zero, we obtain, $V_o=2$.
 If $a_0=a_1=1$ and all other a_i 's are zero, $V_o=2+1=3V$ etc.
 clearly, V_o is an analog voltage proportional to the digital input.

$$\begin{aligned} R &= V/I \\ I &= V/R \\ &= \frac{10V}{10 \times 10^3} \\ &= 1mA \end{aligned}$$

Using the numerical values shown in above figure, we see that if the MSB is 1 and all other bits are 0, then the current through the $10-K$ resistor will be $1mA$ and the output voltage will be $V_o=5 = 16 \times \left(\frac{5}{16}\right) V$. We see that the weight of the LSB (if $N=5$) becomes $V_o = \frac{10}{16} = 1 \times \frac{5}{16} V$.

⇒ If all five bits are 1, the output becomes:
 $V_o = \left(\frac{1}{2} + \frac{1}{4} + \frac{1}{8} + \frac{1}{16} + \frac{1}{32}\right) V_R = \left(1 + \frac{1}{2} + \frac{1}{4} + \frac{1}{8} + \frac{1}{16}\right) \frac{10}{2}$ where $V_R = 10V$
 $V_o = \left(1 + \frac{1}{2} + \frac{1}{4} + \frac{1}{8} + \frac{1}{16}\right) \times 5 = \frac{31}{16} \times \frac{5}{2} = 9.68V$ — (A)

Let $a_0=a_1=a_2=a_3=a_4=1, V_R=10V$

from Eq. (2), $V_o = (16+8+4+2+1) \frac{10}{32} = 31 \times \frac{10}{32} = 9.68V$.

From circuit,

$$\begin{aligned} \frac{1}{R_{eq}} &= \frac{1}{R} + \frac{1}{2R} + \frac{1}{4R} + \frac{1}{8R} + \frac{1}{16R} \\ &= \left(1 + \frac{1}{2} + \frac{1}{4} + \frac{1}{8} + \frac{1}{16}\right) \frac{1}{R} \\ &= \frac{(16+8+4+2+1)}{16} \frac{1}{R} \\ &= \frac{31}{16} \times \frac{1}{10} (k\Omega)^{-1} \\ &= \frac{31}{160} (k\Omega)^{-1} \end{aligned}$$


for inverting O/P amp.

$$\frac{V_o}{V_{in}} = - \frac{R_f}{R_{in}}$$

$$V_o = -V_{in} \frac{R_f}{R_{in}} \rightarrow R_{eq}$$

$$= 10 \times \frac{5 \times 10^3}{160 \times 10^3} \times 31 = \frac{5 \times 31}{16} = \frac{10 \times 31}{32} = 9.68V. \quad \underline{Ans}$$

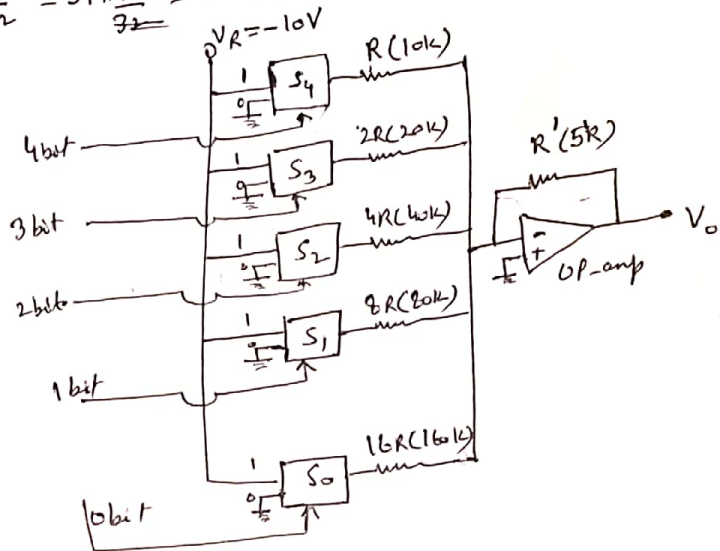We see the value of V_o is same for using Eq. (2) as well as using circuit.
 The accuracy and stability of this D/A converter depend primarily on the absolute accuracy of the resistors and the tracking of each other with temperature.



(B)

Integrated Electronics → Jacob millman + Christos C. Halkias
 Tata McGraw-Hill Publishing Company Limited
 7 west Patel Nagar, New Delhi - 110008.