

Forced Commutation.

- Forced commutation circuits are very important from competition point of view, where questions are asked for finding.

↳ conduction time of thyristors.


↳ turn-off time of thyristors.

↳ circuit turn-off time of thyristors.

↳ peak value of current through thyristor etc.

- So, while studying these topics, pay special attention to above mentioned questions.

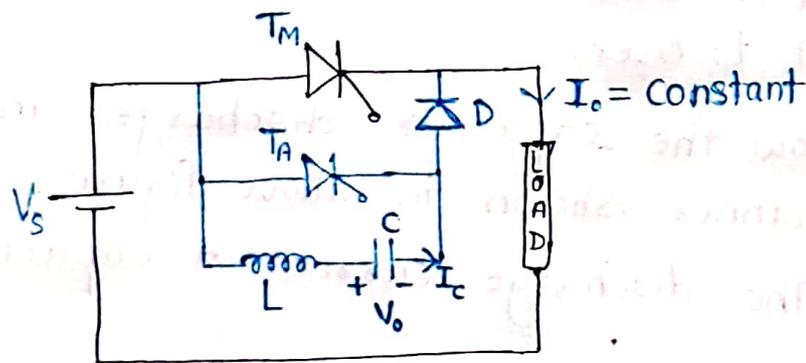(a) Resonant-Pulse Commutation or Current Commutation or Class-B commutation.



Assumptions :-

- 1) Load current is assumed to remain constant at I_o . (i.e. Load is highly inductive).
- 2) Capacitor is initially charged with V_s volts as shown in above figure.
- 3) Before $t = 0$ sec., T_M is in ON state and $I_M = I_o$.

In the above circuit,

T_M → Main thyristor, which needs to be commutated

T_A → Auxiliary thyristor, which helps in commutation of T_M .

D → Diode.

→ Operation of the circuit can be understood in 3-steps.

Step 1 :- At $t=0$ sec. T_A is turned-on, in order to initiate commutation of T_M .

- capacitor has initial voltage V_s , in such a manner that it forward biases T_A .

- T_A is turned on at $t=0$ sec.

- Now the capacitor discharges in the manner shown in above figure.


- The discharge current of capacitor is given by


$$I_c = -I_p \sin \omega t$$

I_p → peak current

I_c → instantaneous value of discharge current.

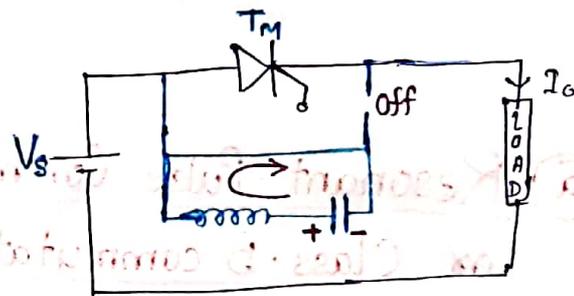- When discharge current decays to zero, the capacitor voltage reverses its polarity.




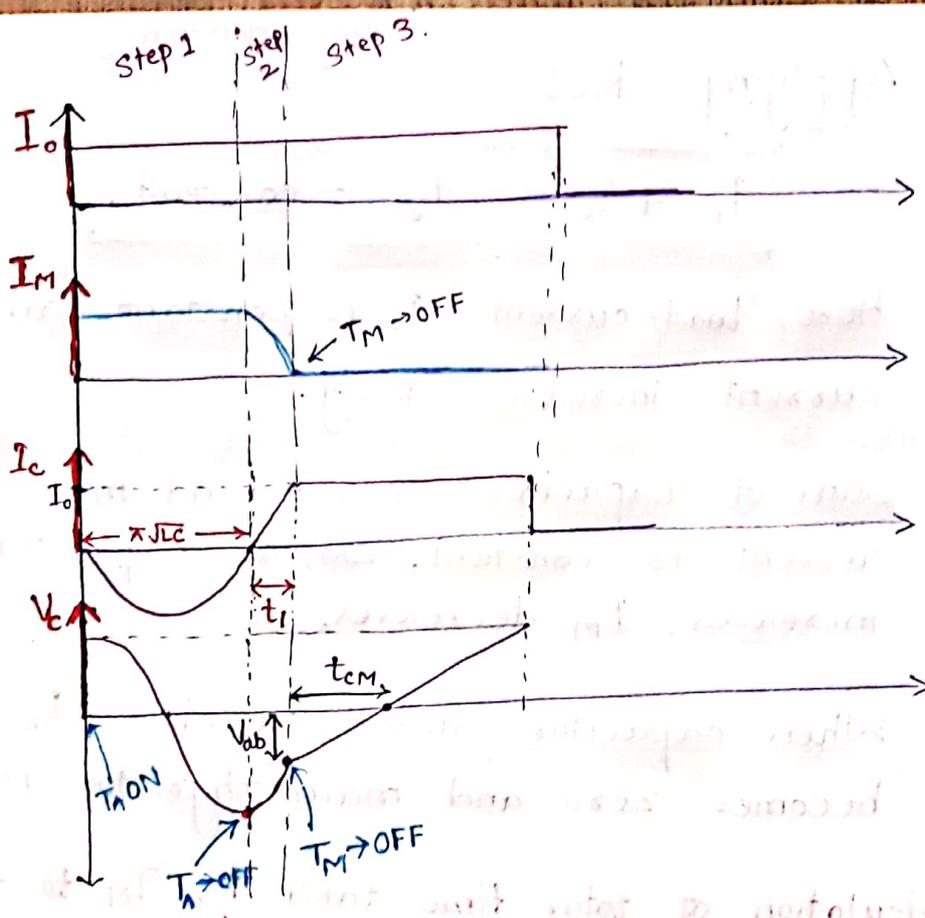

- Capacitor voltage is cosine when I_c is sine function.
- At end of ~~end~~ step 1, capacitor polarity reverses and T_A turns off.
 \hookrightarrow at $\omega_0 t_0 = \pi$

Step 2:- T_A turns-off and diode D turns-on.

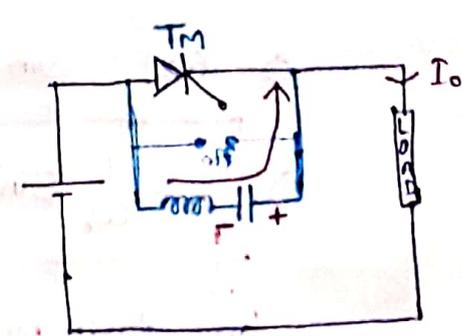- Capacitor polarity has reversed. So, when T_A turns-off, capacitor voltage applies a forward bias across the diode. So, diode ~~is~~ turns on.



- Now, the capacitor current increases from zero to I_0 . (see the waveform for step-2.)

Applying KCL,

$$I_M + I_C = I_o = \text{constant.}$$

- Here, load current I_o is constant and capacitor current increases slowly.
- Sum of capacitor current and main thyristor current is constant. So, as capacitor current increases, I_M decreases.
- When capacitor current reaches I_o , then I_M becomes zero and main thyristor is turned off.

Calculation of total time taken by T_M to turn-off

- Let time taken by capacitor current to reach I_o , after t_o time be t_1 . (shown in waveform).
- T_M is off when $I_C = I_o$.

$$\Rightarrow I_p \sin \omega t_1 = I_o \quad \left(\because I_C = I_p \sin \omega t \right)$$

$$\Rightarrow \sin \omega t_1 = \frac{I_o}{I_p}$$

$$\Rightarrow \omega t_1 = \sin^{-1} \left(\frac{I_o}{I_p} \right)$$

$$\left(I_p = V \sqrt{\frac{C}{L}} \right)$$

↓
Peak current

$$\left(\omega_o = \sqrt{LC} \right)$$

↓
resonant angular freq.

$$\Rightarrow \boxed{t_1 = \frac{1}{\omega_o} \sin^{-1} \left(\frac{I_o}{I_p} \right)} \Rightarrow \boxed{t_1 = \sqrt{LC} \sin^{-1} \left(\frac{I_o}{I_p} \right)}$$

time taken by T_M to switch-off after t_o sec.

So, total time taken by T_M to turn-off from the instant T_M is turned-on at $t=0$

$$= t_o + t_1 = \pi \sqrt{LC} + \sqrt{LC} \sin^{-1} \left(\frac{I_o}{I_p} \right)$$

Important

∴ Total time taken by T_m to turn off ~~the thyristor~~

$$= \pi \sqrt{LC} + \sqrt{LC} \sin^{-1}\left(\frac{I_o}{I_p}\right)$$

- Conduction time of auxiliary thyristor, $T_A = t_o = \pi \sqrt{LC}$

- Peak value of current through auxiliary thyristor $= I_p = V_s \sqrt{\frac{C}{L}}$


- Peak value of current through main thyristor $= I_o$

Step 3:- T_m is already turned off, but we need to maintain reverse bias voltage across it to enable ~~the~~ blocking capability. This reverse bias voltage is maintained in step 3.

- When $I_c = I_o$, T_m has turned off.

- Now, capacitor current I_c remains constant, till the capacitor charges to $+V_s$.

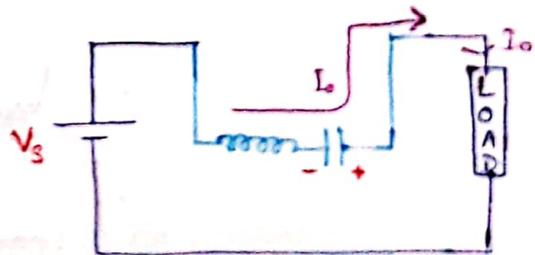- Now capacitor current is no longer sinusoidal. Load is suppressing it and maintaining constant current I_o .



→ To Find Circuit-turn-off time of T_m :-

Capacitor voltage is, $V_c = \frac{1}{C} \int I_c dt$

$I_c = \text{constant}$

Circuit turn-off time is the duration for which reverse bias voltage is applied across the thyristor, to enable it to regain blocking capability.

- In the waveform, t_{cm} represents the circuit turn-off time of main thyristor T_m .
- In the waveform, the value of reverse voltage which appears across the T_m , when it gets turned-off is V_{ab} .

Now, putting the values in the expression for capacitor voltage.

$$V_c = V_{ab} = \frac{1}{C} \int I_o dt$$

$$\Rightarrow V_{ab} = \frac{I_o}{C} \cdot t_{cm}$$

$$\Rightarrow t_{cm} = \frac{V_{ab} \cdot C}{I_o} \quad \underline{\underline{Imp}}$$

- Finding value of V_{ab} .

- Capacitor voltage is a cosine function.

- V_{ab} is capacitor voltage at time t_1 .

$$\begin{aligned} \therefore V_{ab} &= V_c \\ &= V_s \cos \omega t, \end{aligned}$$

$$V_{ab} = V_s \cdot \cos \left\{ \sin^{-1} \left(\frac{I_o}{I_p} \right) \right\}$$

$$\begin{aligned} \therefore \omega t_1 &= \sin^{-1} \frac{I_o}{I_p} \\ \text{and } I_p &= V_s \sqrt{\frac{C}{L}} \end{aligned}$$

∴

$$t_{em} = V_{ab} \frac{C}{I_0}$$

$$V_{ab} = V_s \cos \left(\sin^{-1} \frac{I_0}{I_p} \right)$$

$$I_p = V_s \sqrt{\frac{C}{L}}$$

$$\omega_0 t_1 = \sin^{-1} \frac{I_0}{I_p}$$