

Q.1 A 120V, 100 Watt lamp is to be connected to a 220V, 50Hz AC supply. What value of pure inductance should be connected in series in order to run the lamp on rated voltage.

Solution:



$$V_R = 120V$$

$$V_L = ?$$

$$V_S = V_R + jV_L$$

$$V_S = \sqrt{V_R^2 + V_L^2}$$

$$220V = \sqrt{120^2 + V_L^2}$$

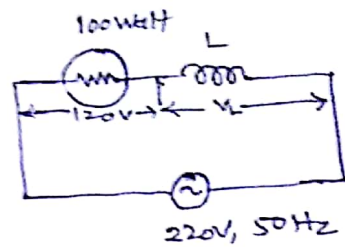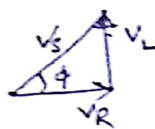

$$V_L = 184.39 \text{ Volt}$$

⇒ Current through the lamp and inductance is same.

$$\text{Current Through lamp } I = \frac{P}{V} = \frac{100}{120} \text{ A}$$

$$V_L = I X_L = I \times 2\pi f L$$

$$L = \frac{V_L}{I \times 2\pi f}$$

$$L = \frac{184.39}{\frac{100}{120} \times 2 \times \pi \times 50}$$

$$L = 0.7046 \text{ H}$$

Q.2 A coil connected to 100V DC supply draws 10 A and the same coil connected 100V, AC voltage of frequency 50 Hz draws 5 A. Calculate the parameters of the coil and power factor.

Sol. Coil means a resistance and inductance both.


$$\text{Let impedance of coil } Z = R + jX_L$$

$$X_L = 2\pi f L$$

① in case of DC  $f = 0$ , Hence  $X_L = 0$

$$\text{Hence resistance of coil } R = \frac{V}{I} = \frac{100}{10}$$

$$R = 10 \Omega$$

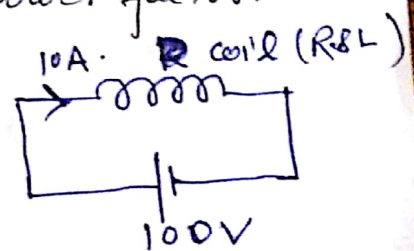


② in case of AC supply impedance of coil

$$|Z| = \frac{V}{I} = \frac{100}{5} = 20 \Omega$$

$$\sqrt{R^2 + X_L^2} = 20 \Rightarrow X_L = 17.32 \Omega$$
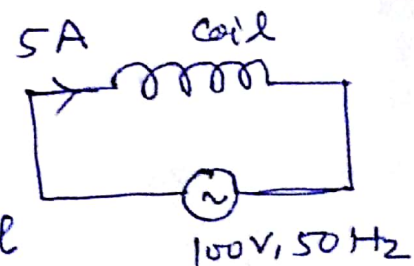
$$\Rightarrow L = \frac{X_L}{2\pi f} = 0.05 \text{ H}$$



$$\begin{aligned} Z &= 20 \\ R &= 10 \\ \cos \phi &= R/Z \\ \cos \phi &= 0.5 \end{aligned}$$

Q.3 A Load having impedance of  $(1+j1) \Omega$  is connected to an ac voltage represented as  $V = 20\sqrt{2} \cos(\omega t + 10^\circ)$  Volt. Find the current in load expressed in the form of


$$i = I_m \sin(\omega t + \phi)$$

$$Z = 1 + j1 = |Z| \angle \phi$$

$$|Z| = \sqrt{1^2 + 1^2} = \sqrt{2}$$

$$\phi = \tan^{-1}\left(\frac{1}{1}\right) = 45^\circ$$

$$Z = \sqrt{2} \angle 45^\circ$$

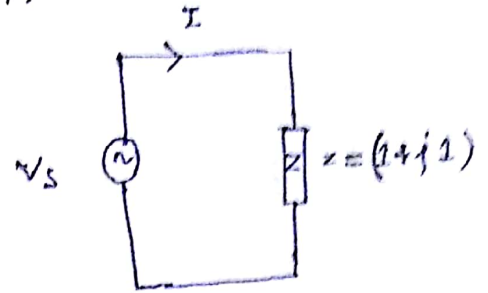

voltage across the load  $V = 20\sqrt{2} \cos(\omega t + 10^\circ)$   
 $= 20\sqrt{2} \sin(\omega t + 100^\circ)$

$$V_{rms} = \frac{V_m}{\sqrt{2}} \angle 100^\circ$$

$$V_{rms} = \frac{20\sqrt{2}}{\sqrt{2}} \angle 100^\circ = 20 \angle 100^\circ$$

Current Through load  $I = \frac{V}{Z} = \frac{20 \angle 100^\circ}{\sqrt{2} \angle 45^\circ}$

$$I = 14.144 \angle 55^\circ \text{ (rms)}$$

$$I_{rms} = 14.144$$

$$I_m = 14.144 \times \sqrt{2} = 20 \text{ and } \phi = 55^\circ$$

$$i = 20 \sin(\omega t + 55^\circ)$$

Q4 A emf is given by  $100 \sin(314t - \frac{\pi}{4})$  volt is applied to a circuit and the current is  $20 \sin(314t - \frac{\pi}{2})$  A. Find (i) frequency (ii) circuit elements.

sol.

$$\omega t = 314t$$

$$2\pi f = 314$$

$$f = 50 \text{ Hz}$$

$$E = \frac{100}{\sqrt{2}} \angle -\frac{\pi}{4} \quad I = \frac{20}{\sqrt{2}} \angle -\frac{\pi}{2} \quad 45^\circ$$

$$Z = \frac{E}{I} = \frac{\frac{100}{\sqrt{2}} \angle -\frac{\pi}{4}}{\frac{20}{\sqrt{2}} \angle -\frac{\pi}{2}} = \frac{100 \angle -60^\circ}{20 \angle -45^\circ} = 5 \angle (90^\circ - 45^\circ) = 5 \angle 45^\circ$$

$$Z = R + jX_L = 5 \cos 45^\circ + j5 \sin 45^\circ$$

$$Z = \frac{5}{\sqrt{2}} (1 + j)$$

$$R = \frac{5}{\sqrt{2}} \Omega, \quad X_L = \frac{5}{\sqrt{2}} \Omega \Rightarrow L = \frac{20}{2\pi} \frac{X_L}{f}$$