

## UNIT-2 (A.C. Circuits)

Ques. 1 > For a given A.C. Voltage

$$V = 200\sqrt{2} \sin(100\pi t - 30^\circ)$$

Find (i) Max value (ii) r.m.s. Value (iii) frequency (iv) Phase angle  
(v) average value (vi) angular velocity (vii) Form & Peak Factor

Ans. >  $V = 200\sqrt{2} \sin(100\pi t - 30^\circ)$

general eq.  $V = V_m \sin(\omega t - \phi)$

on comparing  $\rightarrow V_m = 200\sqrt{2}$

$$\omega = 100\pi$$

$$\phi = 30^\circ$$

(i) Max Value  $V_m = 200\sqrt{2}$

(ii) R.m.s. Value  $V_{rms} = V_m/\sqrt{2} = 200$

(iii)  $\omega = 2\pi f = 100\pi$   
 $f = 50 \text{ Hz.}$

(iv)  $\phi = 30^\circ$  Phase angle =  $30^\circ$

(v)  $V_{av} = \frac{2V_m}{\pi} = \frac{400\sqrt{2}}{\pi}$

(vi). angular velocity  $\Rightarrow \omega = 100\pi \text{ rad/sec.}$

(vii)

$$\text{Form Factor} = \frac{V_{rms}}{V_{av}}$$
$$= \frac{V_m/\sqrt{2}}{2V_m/\pi}$$
$$= 1.11$$

$$\text{Peak Factor} = 1.414$$

Ques. 2 > Explain form factor & Crest or Peak factor.

Ans. > (a) Form Factor  $\rightarrow$  The ratio of Effective or R.M.S. Value to Average Value is known as Form Factor

$$\text{Form Factor} = \frac{\text{R.M.S. Value of A.C.}}{\text{Average Value of A.C.}}$$

(b) Peak Factor  $\rightarrow$  The ratio of Max. Value to R.M.S. Value is known as peak or Crest Factor.


$$\text{Peak Factor} = \frac{\text{Maximum Value of A.C.}}{\text{R.M.S. Value of A.C.}}$$

Ques. 3 > What is The Physical Significance of Phasor. :

Ans. > As we know Alternating quantities change its Magnitude and Direction Continuously so Mathematical analysis of A.C. is very Complicated For Representing A.C. we use Phasor Method for Simplicity of Mathematical analysis

Phasor > Phasor is basically a Rotating line whose Magnitude is equal to R.M.S value of alternating quantity and which is Rotating in anticlockwise direction with angular velocity  $\omega$ .

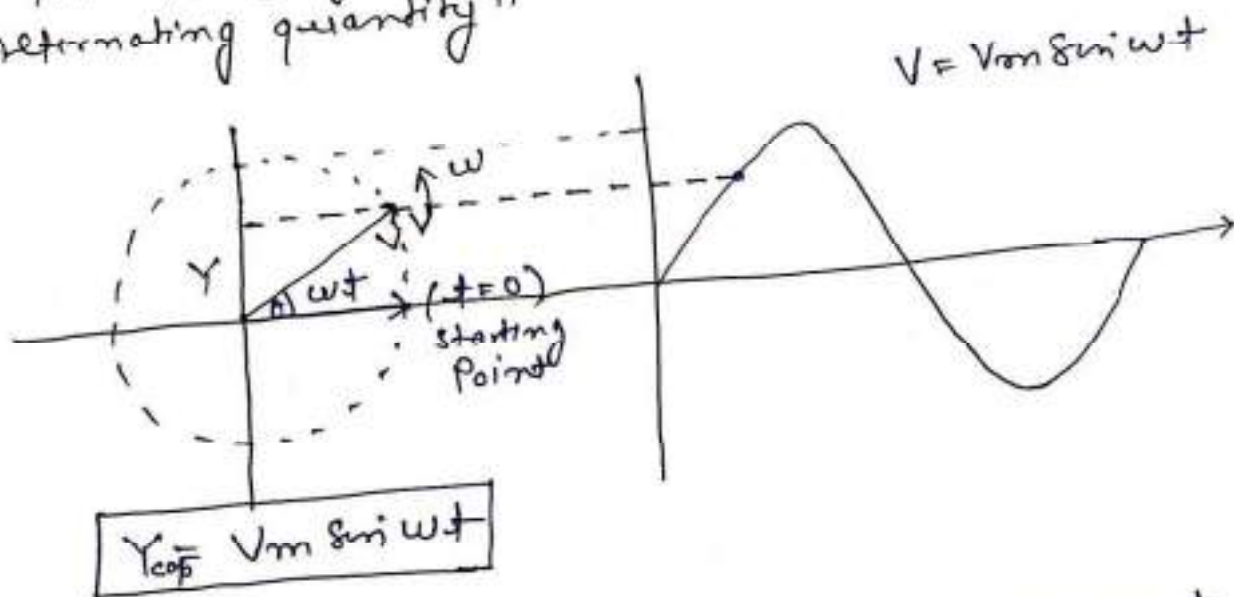" Y component of Phasor gives the Instantaneous Value of particular Alternating quantity, the starting point ( $t=0$ ) of Phasor depend upon the equation of Alternating quantity "



\* For Mathematical Analysis we represent Phasor at ( $t=0$ ) only and this is used for addition and Substraction of alternating quantities.

Ques 4 > Represent following Alternating quantities in phasor form then find the resultant of all.

$$V_1 = 100 \sin 500t$$

$$V_2 = 200 \sin(500t + 45)$$

$$V_3 = -50 \cos 500t$$


Ans. → For analysis all quantities must in phasor form

$$V_1 = 100 \sin 500t$$

$$V_2 = 200 \sin(500t + 45)$$

$$V_3 = 50 \sin(500t - \pi/2)$$

Phasor Representation >

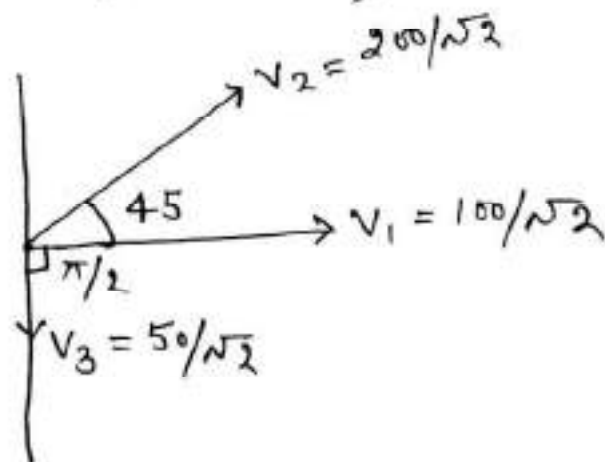

Addition >


	$V_x$	$V_y$
$V_1$	$100/\sqrt{2}$	0
$V_2$	$100\sqrt{2}$	141.42
$V_3$	0	-50
$V_R$	241.42	91.42

$$V_R = \sqrt{V_x^2 + V_y^2} = V_{Rmax} = 258.15 \text{ V}$$

$$\tan \phi = \frac{91.42}{241.42} \quad \phi =$$

Ques. 5) Prove that in purely Inductive & Capacitive ckt Power Consumed is zero.

Ans. > (i) Purely Inductive ckt →

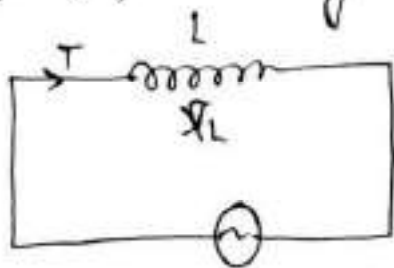

$$V = V_m \sin \omega t$$

the applied voltage and  $i$  is given by

$$e_L = -L \frac{di}{dt}$$

$$V = -e_L$$

$$V = L \frac{di}{dt}$$

$$di = \frac{V}{L} dt$$

Integrating both sides


$$\int di = \int \frac{V}{L} dt$$

$$\int di = \int \frac{V_m \sin \omega t dt}{L}$$

$$I = \frac{V_m}{\omega L} \sin(\omega t - \pi/2)$$

$$I = I_m \sin(\omega t - \pi/2)$$
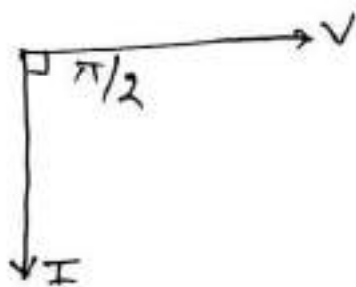
$$I_m = \frac{V_m}{\omega L} = \frac{V_m}{X_L}$$



⇒ When alternating current flows through the inductor an e.m.f. known as self induced e.m.f. is induced across the inductor and this induced e.m.f. opposes

Now Instantaneous Power  $P$

$$P_{in} = VI$$


$$= V_m \sin \omega t I_m \sin(\omega t - \pi/2)$$

$$P_{in} = \frac{V_m I_m}{2} \sin 2\omega t$$

$$\boxed{P_{av} = 0}$$

because average value of  $\sin 2\omega t$  in half cycle is zero.

(ii) Purely Capacitive circuit

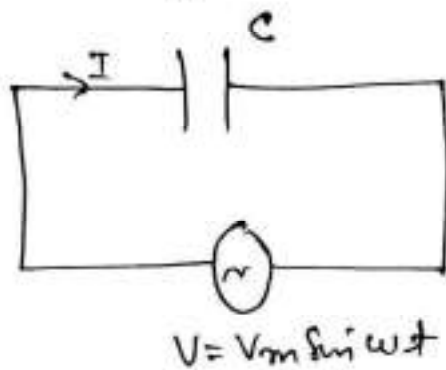

at particular time charge stored in capacitor is given by

$$Q = eV$$

$$Q = C V_m \sin \omega t$$

now

$$I = \frac{dQ}{dt}$$

$$I = \frac{d}{dt} (C V_m \sin \omega t) = V_m \omega C \cos \omega t$$

$$I = V_m \omega C \sin(\omega t + \pi/2)$$

$$I = \frac{V_m}{1/\omega C} \sin(\omega t + \pi/2) = \frac{V_m}{X_c} \sin(\omega t + \pi/2)$$

where  $X_c \rightarrow$  Capacitive reactance

\* Now instantaneous power across capacitor


$$\begin{aligned} P_{in} &= V I \\ &= V_m \sin \omega t I_m \sin(\omega t + \pi/2) \\ &= \frac{V_m I_m}{2} (\sin \omega t \cos \omega t) \end{aligned}$$

$$P_{in} = \frac{V_m I_m}{2} \sin 2\omega t$$

+ now average power  $\rightarrow$


$$P_{av} = 0$$

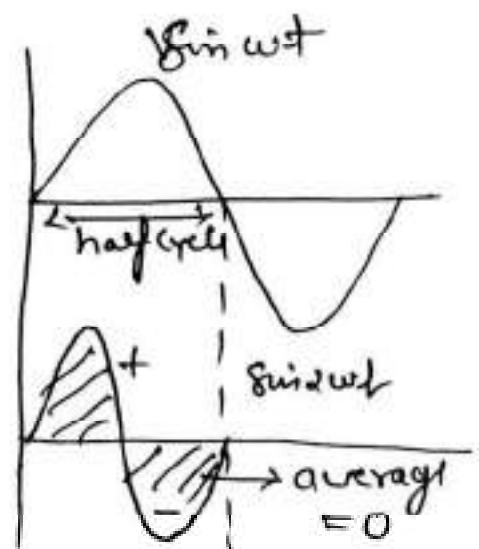because average value of  $\sin 2\omega t$  in half cycle is zero




Ques. 6 → Explain Impedance Triangle with Suitable Diagram.

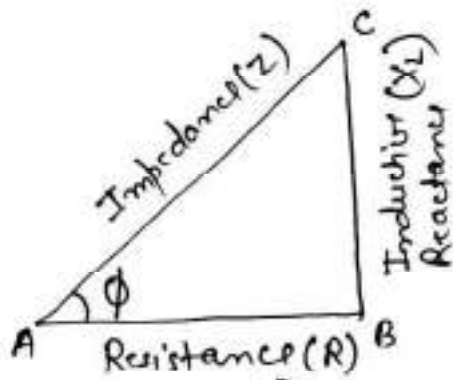Ans. → When Resistance, Inductance and Impedance are represented by three sides of right-angled triangle. Such a triangle is known as Impedance Triangle.


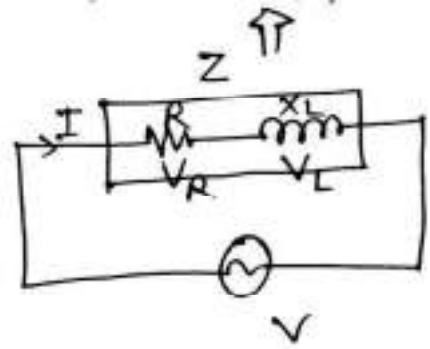
$$\left. \begin{aligned} AB &= \frac{V_R}{I} = R \\ BC &= \frac{V_L}{I} = X_L \\ AC &= \frac{V}{I} = Z \end{aligned} \right\}$$



\* the angle b/w AB & AC is known as Phase angle

$$\cos \phi = R/Z$$

\*  $\cos \phi$  is the Power Factor of the circuit.

Ques. 7 → Discuss about Apparent, True and Reactive Power.

Ans. → (i) Apparent Power → The product of rms value of voltage & current is known as Apparent Power.  $P_a = VI$  unit → V-A or KVA (Volt-Ampere)


(ii) True Power → When Apparent Power is multiplied by power factor then this product is known as True Power.  $P_T = VI \cos \phi$  unit → W or kW (Watt) or (kilowatt)

(iii) Reactive Power → The product of Apparent Power to the sine of angle b/w voltage and current is known as Reactive Power.  $P_R = VI \sin \phi$  unit → VA or KVAR (Volt-Ampere Reactive)


Ques 8 → Explain Power Triangle the Discuss about Watt and Wattless Component of Current.

Ans. →

$I \cos \phi$  → active Component

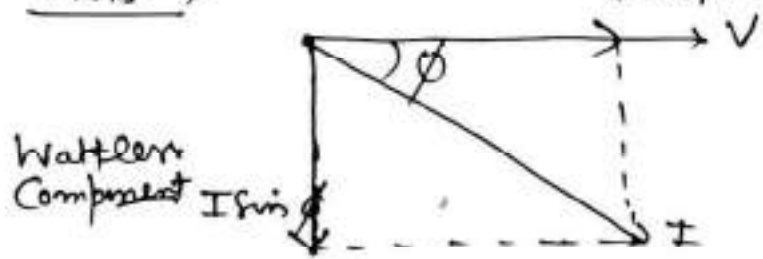

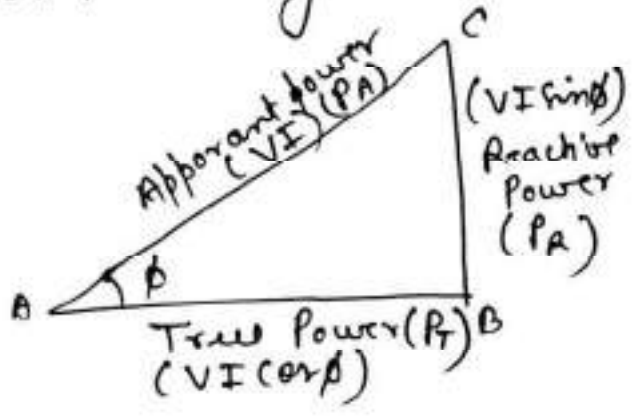
- \* The Component of current in phase with Voltage is known as active component or in Watt Component of current because it is responsible for power consumption.
- \* Wattless Component → The Component of current quadrature to Voltage is called Wattless Component it does not consume any power.



$$P_A = \sqrt{P_T^2 + P_R^2}$$

Ques 9 → Explain Choke coil then define quality Factor.

Ans. →

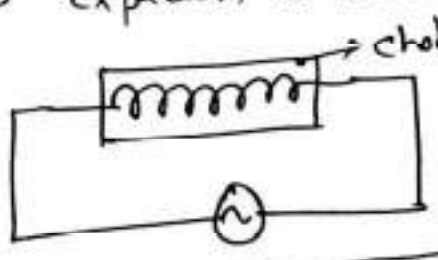

" A coil having high inductance and low resistance is known as choke coil "

$$\text{Power loss in choke coil} = \text{Iron-loss} + \text{Copper-loss}$$

Q Factor → Reciprocal of Power Factor is known as quality Factor

$$Q = \frac{1}{\cos \phi}$$


" The quality Factor of choke coil is very high because  $\phi \rightarrow 90^\circ$  "

Ques. 9 → A coil having Resistance  $6\Omega$  and Inductance  $0.0255\text{ H}$  is connected across  $230\text{ V}$ ,  $50\text{ Hz}$ .

A.C. Supply Calculate:

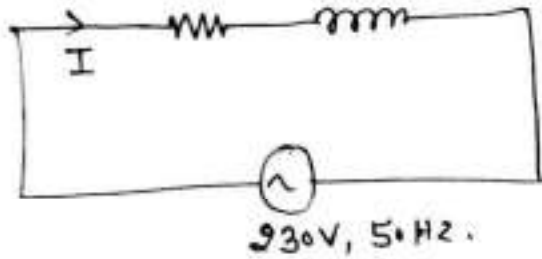- (i) Impedance of coil (ii) Current in circuit (iii) Power factor  
 (iv) Power consumed (v) Instantaneous Value of Voltage & Current  
 (vi) Apparent & Reactive power

Ans. →  $R = 6\Omega$   $L = 0.0255\text{ H}$



$$X_L = 2\pi fL$$

$$= 2 \times 3.14 \times 50 \times 0.0255$$


$$= 8\Omega$$

(i)  $Z = \sqrt{R^2 + X_L^2} = \sqrt{6^2 + 8^2} = 10\Omega$

(ii)  $I = V/Z = \frac{230}{10} = 23\text{ A}$

(iii)  $\cos\phi = R/Z = 0.6$   $\phi = 53$

(iv)  $P = VI \cos\phi$   
 $= 230 \times 23 \times 0.6 = 3174\text{ W}$

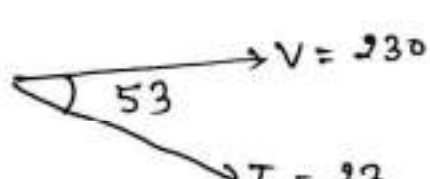(v) 

$$V = 230\sqrt{2} \sin \omega t$$

$$I = 23\sqrt{2} \sin(\omega t - 53)$$

(vi) Apparent & Reactive Power

⇒ Apparent  $P_A = VI$   
 $= 230 \times 23 = 5290\text{ VA}$   
 $\underline{5.290\text{ KVA}} \text{ Ans.}$

⇒ Reactive power =  $VI \sin\phi$   
 $= 230 \times 23 \times 0.8$   
 $= 4232\text{ VAR}$   
 $\underline{4.232\text{ KVAR}} \text{ Ans.}$



Ques. 10 → The Instantaneous Value of Voltage and Current in particular circuit is given by



$$V = 283 \sin 314t$$

$$I = 4 \sin (314t - 45^\circ)$$

find (i) Circuit elements & their Value

(ii) Power factor and Power Consumed by ckt.

Ans. →

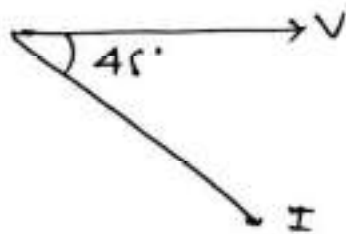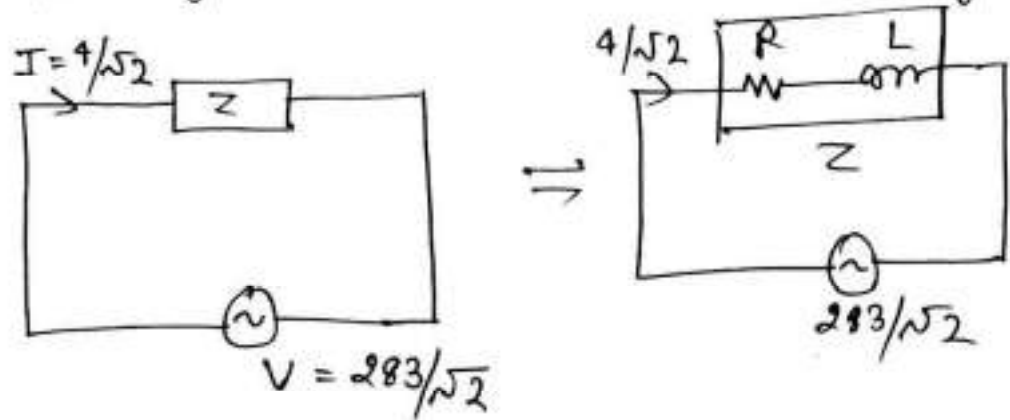

The current is lag behind the supply voltage by  $45^\circ$  so circuit contains R & L

now 
$$Z = \frac{V}{I} = \frac{\frac{283}{\sqrt{2}}}{\frac{4}{\sqrt{2}}} = \underline{70.75 \Omega}$$

$$\begin{aligned} \cos \phi &= \frac{R}{Z} \text{ so } R = Z \cos \phi \\ &= 70.75 \cos 45 \\ &= 50 \Omega \end{aligned}$$

$$\begin{aligned} X_L &= Z \sin \phi \\ &= 50 \Omega \end{aligned}$$

$$2\pi fL = 50 \Omega \Rightarrow L = \frac{50}{2\pi f} = \underline{0.159 H}$$

(ii) Power Factor  $\Rightarrow \cos \phi = \cos 45 = 0.707$  (lagging)

$$\begin{aligned} P &= VI \cos \phi \\ &= \frac{283}{\sqrt{2}} \times \frac{4}{\sqrt{2}} \times 0.707 \end{aligned}$$