

Ques. 1 > Explain Different type of Magnetic Material

Ans. > Magnetic Materials are basically three types

- (i) Paramagnetic Material
- (ii) Diamagnetic Material
- (iii) Ferromagnetic Material

(i) Paramagnetic Materials > The materials which are not strongly attracted by a magnet are known as Paramagnetic material.


Ex. → aluminium, platinum, magnesium.

(ii) Diamagnetic Materials > The materials which are repelled by a magnet such as zinc, mercury, lead are known as Diamagnetic materials.

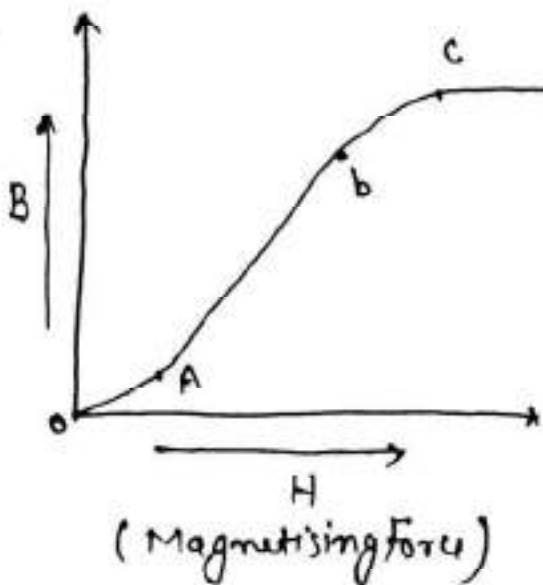(iii) Ferromagnetic Materials > The material which are strongly attracted by a magnet such as Iron, steel, Nickel are known as ferromagnetic materials.

Ques. 2 > Explain B-H curve in detail >

Ans. > The Curve Drawn b/w Induction density B and Magnetising Force H is known as B-H curve or magnetising curve.



* in region OA increase in flux density is very small

* in region ab flux density is directly proportional to magnetising force

* in region bc again increase in flux density is very small.


* beyond c there is no change in flux density on increasing the magnetising force this region is known as magnetic saturation.

Ques-3 > Explain Ideal & Practical Transformer.


Ans. > For a Ideal Transformer we take following assumption's →

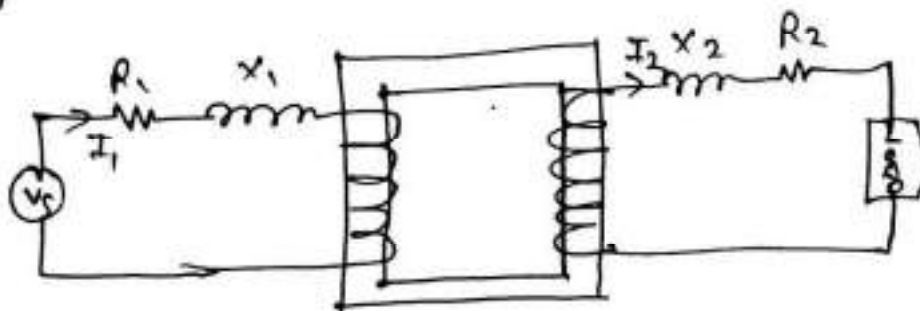- (i) No winding resistance → The primary & Secondary winding's have no resistance.
- (ii) No magnetic leakage → There is no leakage flux all the flux setup is confined to the core.
- (iii) No Iron loss → There is no hysteresis and eddy current loss.
- (iv) Zero magnetising current → The core has infinite permeability and zero reluctance.

Practical Transformer > The Transformer which not follow the assumption of ideal transformer is known as practical transformer.



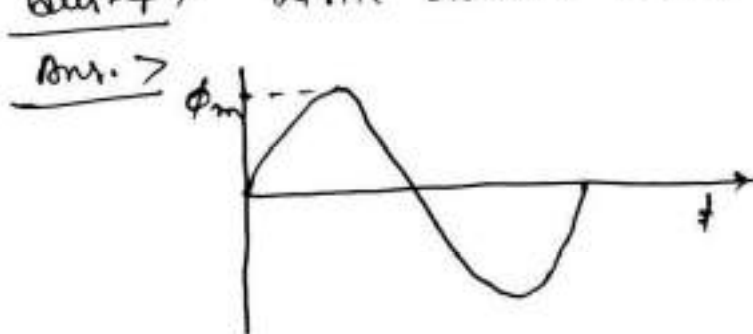Ques-4 > Write down E.m.f. Equation of transformer



* Let flux associated with the core is

$$\phi = \phi_m \sin \omega t$$

* N_1 & N_2 no. of turns in primary and secondary winding.

* Now Induced e.m.f. in Primary winding

$$E_1 = -N_1 \frac{d\phi}{dt} = -N_1 \omega \phi_m \cos \omega t$$

$$= N_1 \omega \phi_m \sin(\omega t - \pi/2)$$

Similarly

$$E_2 = -N_2 \frac{d\phi}{dt}$$

$$= -N_2 \frac{d}{dt} (\phi_m \sin \omega t)$$

$$= N_2 \omega \phi_m \sin(\omega t - \pi/2)$$

Now ~~average~~ ^{r.m.s.} value of induced e.m.f.

$$E_1 = \frac{N_1 \phi_m \omega}{\sqrt{2}}$$


$$= \frac{N_1 \phi_m 2\pi f}{\sqrt{2}}$$

$$E_1 = 4.44 f \phi_m N_1 \text{ Volt}$$

$$E_2 = 4.44 f \phi_m N_2 \text{ Volt}$$

Ques 5 > Draw and Explain Equivalent circuit of Transformer.

Ans. >

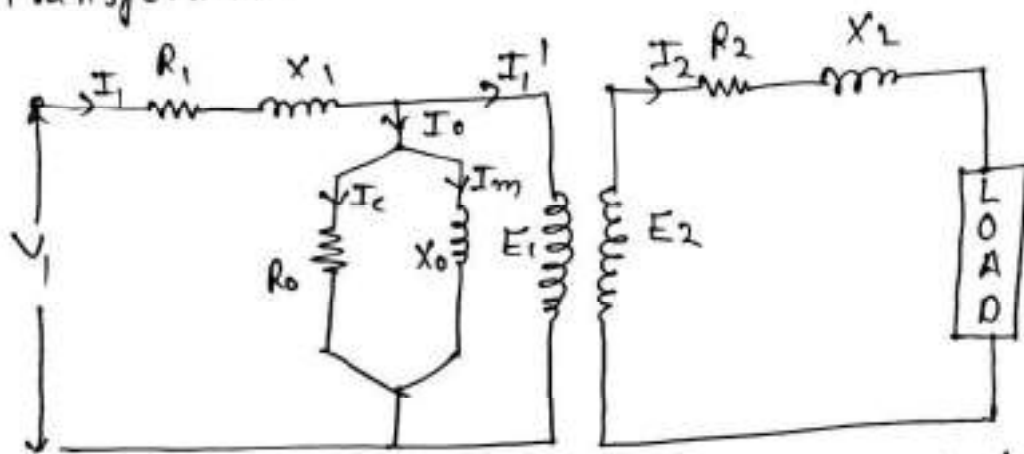

Equivalent ckt of any device can be quite helpful in pre determination of the behavior of the device under various condition of operation.

$R_1, X_1 \rightarrow$ Primary Resistance and Reactance

$R_2, X_2 \rightarrow$ Secondary Resistance and Reactance.

$I_1, I_2 \rightarrow$ Primary & Secondary current

$R_0, X_0 \rightarrow$ No-load parameter of Transformer.

$I_0 \rightarrow$ No-load current

I_1' → Counter balancing current which neutralizes the flux produced by secondary current.

$$I_1 = I_0 + I_1'$$

$$\boxed{N_1 I_1 = N_2 I_2}$$

Ques 6 → Explain Different type of losses present in Transformer.

Ans. → There are two type of losses present in Transformer

(i) Copper loss

(ii) Iron loss

Copper loss → Copper loss is basically due to resistance and it takes place in primary & secondary winding.

$$\boxed{P_c = I_1^2 R_1 + I_2^2 R_2}$$

Iron loss → Iron loss is also two types.

(i) Hysteresis loss

(ii) Eddy current loss.

(i) Hysteresis loss → When alternating flux setup in the core the hysteresis loop is traced out and area under hysteresis loop represent hysteresis loss. and it is given by

$$\boxed{P_h = \eta (B_{max})^n f V \text{ Joule}}$$

where η → Hysteresis coefficient

B_{max} → Max. flux density

f → Supply frequency

V → Volume of core.

(ii) Eddy current loss → When variable flux setup in the core the flux linkage with iron core is change due to which a current is

Induced in the core this current is known as Eddy Current and result heating loss which is known as Eddy current loss. and is given by

$$P_e = K_e (B_{max})^2 f^2 t^2 v \text{ Watt}$$

Ques. 7 → What is the efficiency of Transformer. Derive the expression for max. efficiency.

Ans. 7 → The efficiency of any machine is given by

$$\eta = \frac{\text{output}}{\text{Input}} = \frac{\text{output}}{\text{output} + \text{losses}}$$

for a fixed Input Voltage Iron-loss is constant but Copper loss is depend upon Load current

$$\eta = \frac{\text{output}}{\text{output} + \text{Copper loss} + \text{Iron loss}}$$

let $P_o \rightarrow$ output Power at full load

$P_i \rightarrow$ Iron loss

$P_c \rightarrow$ Copper loss at full load

then efficiency at x -load where x is fraction of full load \rightarrow

$$\eta = \frac{x P_o}{x P_o + P_i + x^2 P_c}$$

for max. efficiency

$$\frac{d\eta}{dx} = 0 \text{ now } \frac{d\eta}{dx} = \frac{(x P_o + x^2 P_c + P_i) P_o - x P_o (1 + 2x P_c)}{(x P_o + P_i + x^2 P_c)^2}$$

$$P_i - x^2 P_c = 0$$

$$x = \sqrt{\frac{P_i}{P_c}}$$

Ques. 8 → In a 25 kVA 2000V/200V Transformer
 The Iron and Copper losses are 200W and
 400W respectively calculate the efficiency at half
 load 0.8 Power Factor lagging, also determine
 max. efficiency and corresponding load.

Ans. → $P_c = 400 \text{ W} = 0.4 \text{ kW}$
 $P_i = 200 \text{ W}$

$$P_o = \frac{1}{2} \times V \times I \times \cos\phi$$

$$= \frac{1}{2} \times 25 \times 0.8$$

$$= 10 \text{ kW}$$

* Copper loss at half-load = $\left(\frac{1}{2}\right)^2 \times 400 = 0.1 \text{ kW}$

* efficiency at half-load →

$$\% \eta = \frac{10}{10 + 0.1 + 0.2} \times 100 = 97.08\%$$


* for max efficiency $x = \sqrt{\frac{P_i}{P_c}}$

$$\text{Corresponding load} = 25 \times \sqrt{\frac{P_i}{P_c}} = 17.68 \text{ kVA}$$

$$\text{So max. efficiency} = \frac{17.68}{17.68 + 0.2 + 0.2} = 97.788\%$$

Ques. 9 → What is Auto Transformer. How Conducting
 Material saved in Auto Transformer.

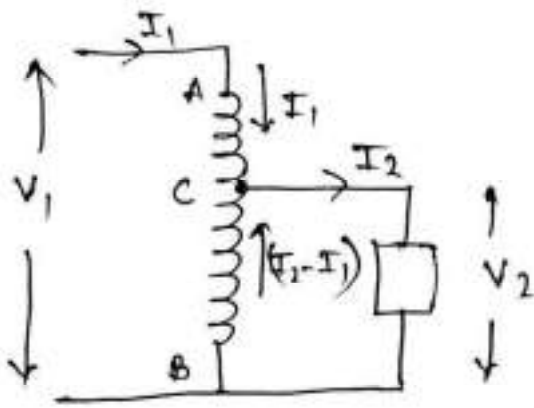Ans. → The Auto Transformer has same principal
 as like conventional two winding transformer
 the only difference is that in auto transformer
 primary and secondary windings are interrelated.



$$\frac{V_2}{V_1} = \frac{E_{BC}}{E_{AB}} = \frac{N_2}{N_1} = \frac{I_1}{I_2} = K$$

Conducting Material → Conducting material required is directly proportional to cross-sectional area and length of conductor so.

Conducting Material in ordinary Transformer

$$C_0 \propto (N_1 I_1 + N_2 I_2)$$

$$C_0 \propto 2N_1 I_1 \quad \text{because } N_1 I_1 = N_2 I_2$$

In auto Transformer

$$C_A \propto I_1 (N_1 - N_2) + N_2 (I_2 - I_1)$$

$$C_A \propto 2(N_1 - N_2) I_1$$

now

$$\frac{C_A}{C_0} = \frac{2(N_1 - N_2) I_1}{2N_1 I_1} = 1 - \frac{N_2}{N_1} = 1 - K$$

$$C_A = C_0 (1 - K)$$

Conducting Material saved.

$$C_0 - C_A = C_0 - C_0 (1 - K)$$

$$= C_0 K$$

$$\text{Saving} = K \times \text{Conducting Material in Ordinary}$$