



**Properties of Hurwitz Polynomials**

- ❖ For all real values of s value of the function P(s) should be real.
- ❖ The real part of every root should be either zero or negative.
- ❖ Let us consider the coefficients of denominator of F(s) is  $b_n, b_{(n-1)}, b_{(n-2)}, \dots, b_0$ . Here it should be noted that  $b_n, b_{(n-1)}, b_0$  must be positive and  $b_n$  and  $b_{(n-1)}$  should not be equal to zero simultaneously.

**Transfer Functions:**

Transfer Impedance Function:

- It is defined as the ratio of Laplace transform of voltage at one port and current at another port.

$$Z_{12}(s) = \frac{V_1(s)}{I_2(s)} \quad \text{and} \quad Z_{21}(s) = \frac{V_2(s)}{I_1(s)}$$

Transfer Admittance Function:

- It is defined as the ratio of Laplace transform of current at one port and voltage at another port.

$$Y_{12}(s) = \frac{I_1(s)}{V_2(s)} \quad \text{and} \quad Y_{21}(s) = \frac{I_2(s)}{V_1(s)}$$

**Driving point functions:**

Driving point admittance functions

- The ratio of Laplace transform of current and voltage at port 1-1' or 2-2' is defined as driving point admittance function.
- Thus there are two driving point admittance functions.
- At port 1-1' denoted as  $Y_{11}(s)$

$$Y_{11}(s) = \frac{I_1(s)}{V_1(s)}$$

- At port 2-2' denoted as  $Y_{22}(s)$

$$Y_{22}(s) = \frac{I_2(s)}{V_2(s)}$$

**Network functions for Two-Port Network are as follows:**

1. Driving point functions:
  - Driving point impedance functions
  - Driving point admittance functions
2. Transfer Functions:
  - Voltage transfer functions
  - Current transfer functions
  - Transfer impedance functions
  - Transfer admittance functions