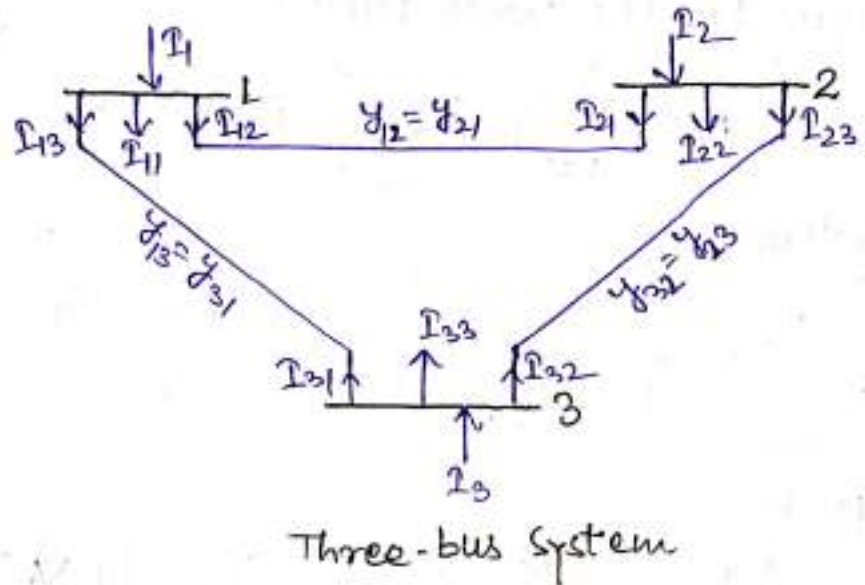


Nodal Admittance Matrix (5)

The load flow equations, using nodal admittance formulation for a three-bus system are developed first and then they are generalized for an n-bus system



At node 1

$$\begin{aligned}
 P_1 &= I_{11} + I_{12} + I_{13} \\
 &= V_1 y_{11} + (V_1 - V_2) y_{12} + (V_1 - V_3) y_{13} \\
 &= V_1 y_{11} + V_1 y_{12} - V_2 y_{12} + V_3 y_{13} - V_3 y_{13} \\
 &= V_1 (y_{11} + y_{12} + y_{13}) - V_2 y_{12} - V_3 y_{13}
 \end{aligned}$$

$$P_1 = V_1 Y_{11} + V_2 Y_{12} + V_3 Y_{13} \quad \longrightarrow \textcircled{1}$$

Here y_{11} is the shunt charging admittance at bus 1 and ground.

$$\begin{aligned}
 Y_{11} &= y_{11} + y_{12} + y_{13} \\
 Y_{12} &= -y_{12}, \quad Y_{13} = -y_{13}
 \end{aligned}$$

Similarly nodal current equations for the other nodes can be written as follows -

$$I_2 = V_1 Y_{21} + V_2 Y_{22} + V_3 Y_{23} \quad \longrightarrow \textcircled{2}$$

$$I_3 = V_1 Y_{31} + V_2 Y_{32} + V_3 Y_{33} \quad \text{--- (3)} \quad \textcircled{6}$$

These equations can be written in a matrix form as follows -

$$\begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} & Y_{13} \\ Y_{21} & Y_{22} & Y_{23} \\ Y_{31} & Y_{32} & Y_{33} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$

--- (4)

$$\begin{aligned} Y_{12} &= -Y_{21} \\ Y_{31} &= Y_{13} = -Y_{13} \\ Y_{21} &= -Y_{12} \\ Y_{32} &= Y_{23} = -Y_{23} \end{aligned}$$

Generalise eqn. for the node current

$$I_p = \sum_{q=1}^3 Y_{pq} V_q, \quad p = 1 \text{ to } 3 \quad \text{--- (5)}$$

For n-Bus system


$$I_p = \sum_{q=1}^n Y_{pq} V_q, \quad p = 1, 2, \dots, n$$

In matrix form

$$\begin{bmatrix} I_1 \\ I_2 \\ \vdots \\ I_n \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} & \dots & Y_{1n} \\ Y_{21} & Y_{22} & & Y_{2n} \\ \vdots & \vdots & & \vdots \\ Y_{n1} & Y_{n2} & \dots & Y_{nn} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ \vdots \\ V_n \end{bmatrix}$$

It can be shown that the nodal admittance matrix is a sparse matrix (a few no. of elements are non-zero) for an actual power system.

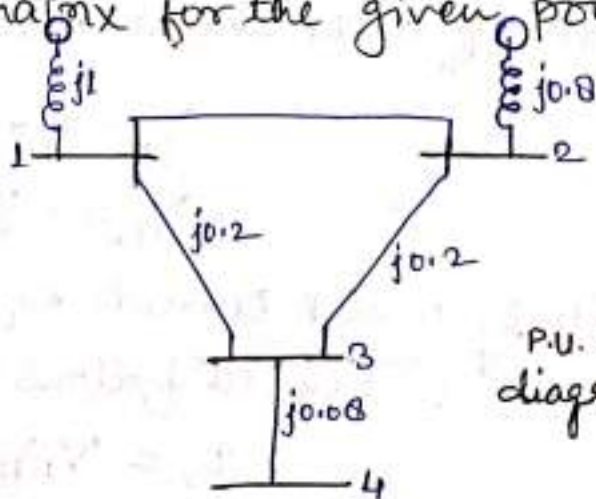Find the admittance matrix for the given power system network.




$$Y_{BUS} = \begin{bmatrix} Y_{11} & Y_{12} & Y_{13} & Y_{14} \\ Y_{21} & Y_{22} & Y_{23} & Y_{24} \\ Y_{31} & Y_{32} & Y_{33} & Y_{34} \\ Y_{41} & Y_{42} & Y_{43} & Y_{44} \end{bmatrix}$$

P.U. impedance diagram of P.S. N/W

Since the nodal solution is based upon ~~Kir~~ Kirchhoff's current law, impedances are converted to admittances i.e.
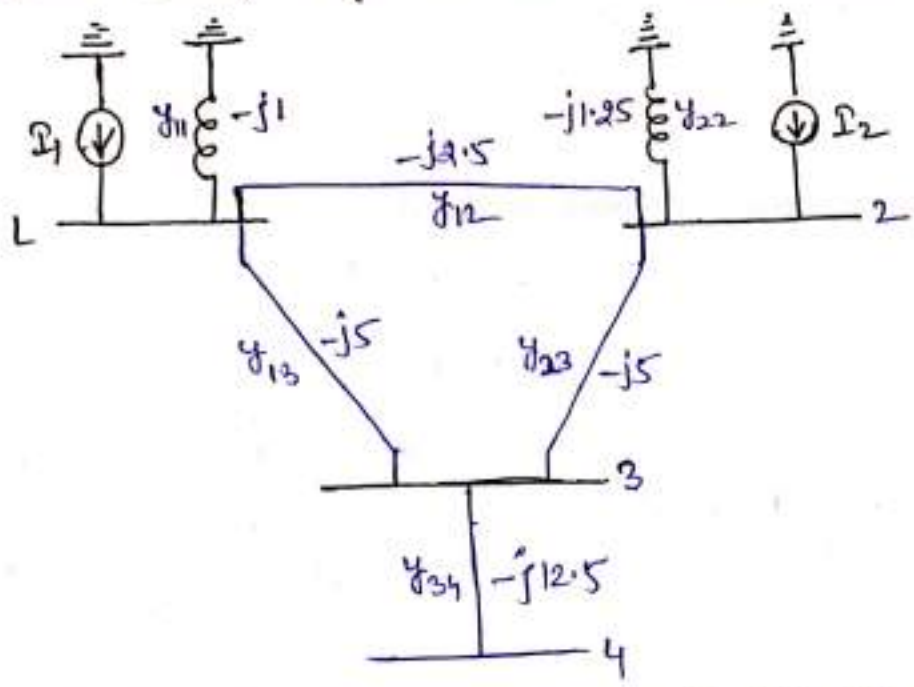
$$Y_{ij} = \frac{1}{Z_{ij}} = \frac{1}{R_{ij} + jX_{ij}}$$



$$Y_{11} = Y_{11} + Y_{12} + Y_{13} + Y_{14}$$

$$= -j1 + (-j2.5) - j5 + 0$$

$$= -j0.5$$

$$Y_{22} = Y_{21} + Y_{22} + Y_{23} + Y_{24}$$

$$= -j2.5 - j1.25 - j5 + 0$$

$$= -j0.75$$

$$Y_{33} = Y_{31} + Y_{32} + Y_{33} + Y_{34}$$

$$= -j5 - j5 + 0 - j12.5$$

$$= -j22.5$$

$$Y_{44} = Y_{41} + Y_{42} + Y_{43} + Y_{44}$$

$$= 0 + 0 - j12.5 + 0$$

$$= -j12.5$$

$$Y_{12} = +j2.5 \quad Y_{13} = +j5, \quad Y_{14} = 0$$

$$Y_{21} = +j2.5 \quad Y_{23} = +j5, \quad Y_{24} = 0$$

$$Y_{31} = +j5 \quad Y_{32} = +j5, \quad Y_{34} = +j12.5$$

$$Y_{41} = 0 \quad Y_{42} = 0, \quad Y_{43} = +j12.5$$

$$Y_{bus} = \begin{bmatrix} -j0.5 & +j2.5 & +j5 & 0 \\ +j2.5 & -j0.75 & +j5 & 0 \\ +j5 & +j5 & -j22.5 & +j12.5 \\ 0 & 0 & +j12.5 & -j12.5 \end{bmatrix}$$

LOAD FLOW PROBLEM FORMULATION —

The complex power injected by the source into the i^{th} bus of a power system is -

$$S_i^o = P_i^o + jQ_i^o = V_i \cdot I_i^* \quad i = 1, 2, \dots, n \quad \rightarrow \textcircled{1}$$

Where V_i \rightarrow voltage at i^{th} Bus w.r.t. ground

I_i \rightarrow source current injected into the Bus.

The load flow problem is handled more conveniently by use of I_i rather than I_i^* . Therefore, taking the complex conjugate of equ. $\textcircled{1}$

$$P_i - jQ_i^o = V_i^* I_i \quad \rightarrow \textcircled{2}$$

As we know that

$$I_i = \sum_{k=1}^n Y_{ik} V_k \quad \rightarrow \textcircled{3}$$

Use equ. no. $\textcircled{3}$ in $\textcircled{2}$

$$P_i - jQ_i^o = V_i^* \sum_{k=1}^n Y_{ik} V_k \quad i = 1, 2, \dots, n \quad \rightarrow \textcircled{4}$$

Equating real and imaginary parts

$$P_i = \text{Re} \left\{ V_i^* \sum_{k=1}^n Y_{ik} V_k \right\} \quad \rightarrow \textcircled{5}$$

$$Q_i = -\text{Im} \left\{ V_i^* \sum_{k=1}^n Y_{ik} V_k \right\} \quad \rightarrow \textcircled{6}$$