

8254 (8253) Programmable Interval Timer

8254 generates accurate time delays & can be used for applications such as a real-time clock, an event counter, a digital one shot, a square wave generator, and a complex waveform generator.

The 8254 includes 3 identical 16 bit counters that can operate independently in any one of the six modes. It is packaged in a 24 dip pin DIP and requires a single +5V power supply.


To operate a counter, 16 bit count is loaded in its register & on command, begins to decrement the count until it reaches 0. At the end of the count, it generates a pulse that can be used to interrupt the MPU.

The 8254 is an upgraded version of 8253, & they are pin compatible. The features of these two devices are almost identical except that.

- 1) 8254 can operate with higher clock frequency range (DC to 8MHz & 10MHz for 8254-2) & the 8253 can operate with clock frequency from DC to 2MHz.

2) The 8254 includes a Status Read-Back Command that can latch the count & the status of the counters.


Pin diagram

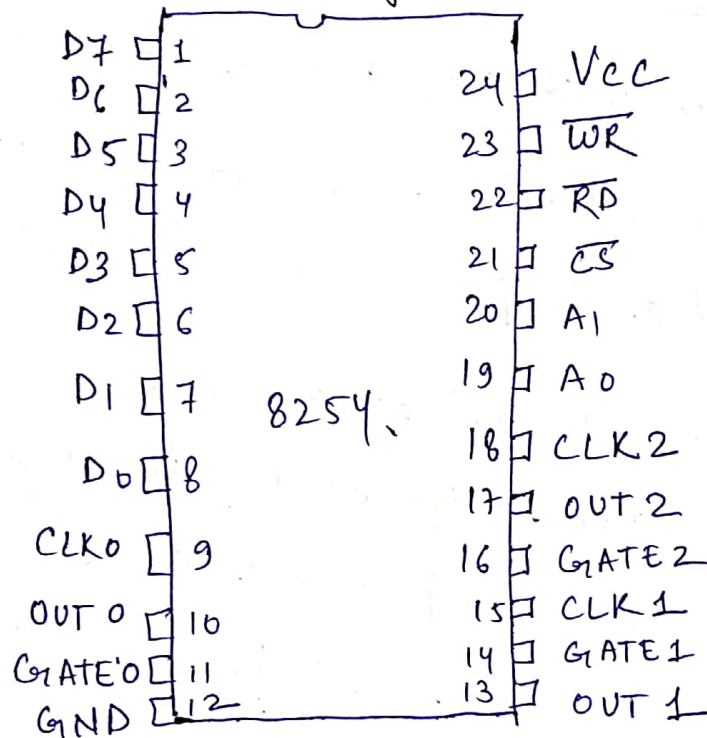

Block diagram of the 8254

It includes three counters (0, 1 & 2), a data bus buffer, Read/Write control logic, & a control register. Each counter has two input signals — clock (CLK) & gate & one output signal — OUT.

Block diagram

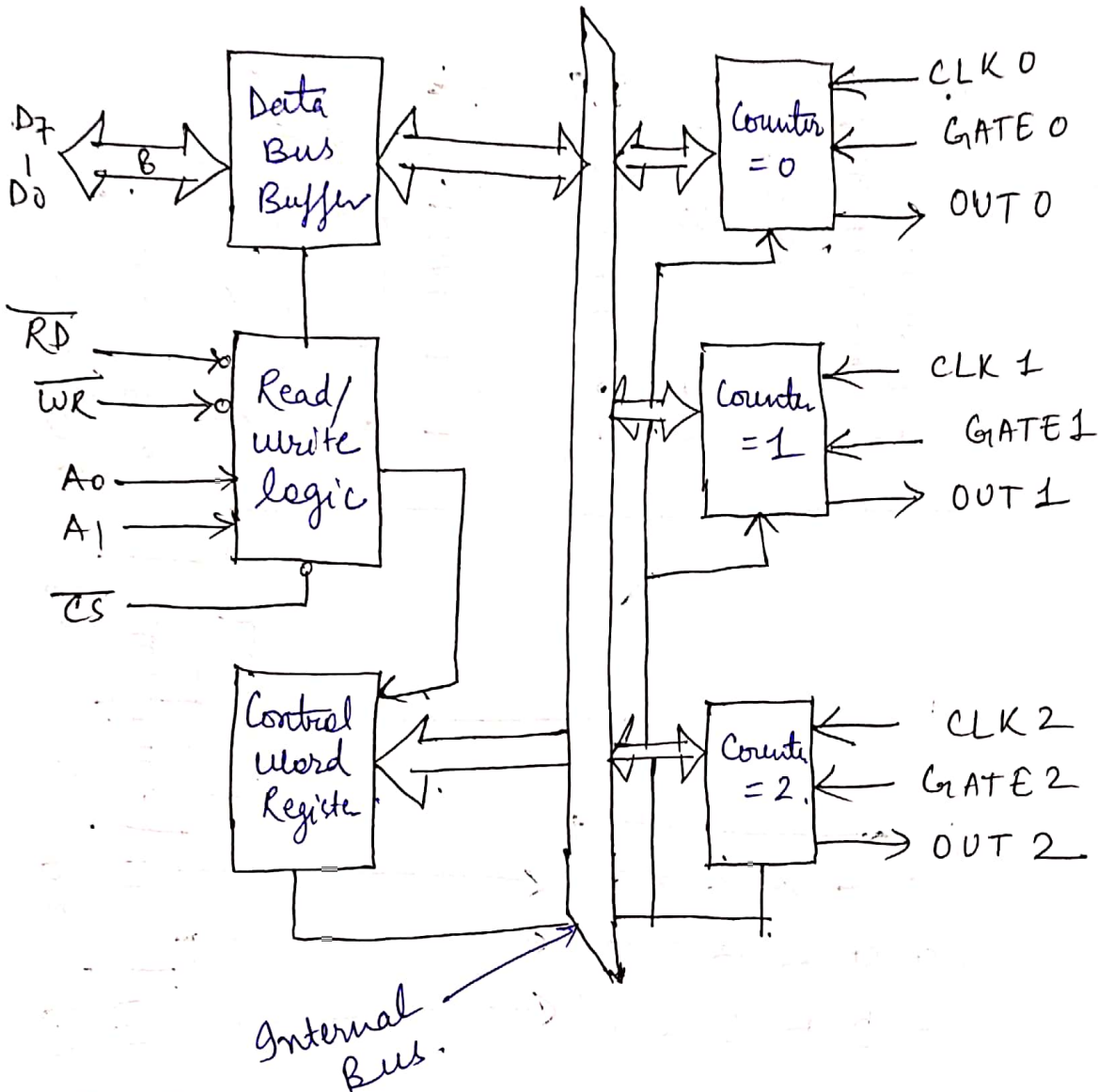


Addressing & format of Mode Control


Register

| \overline{CS} | A ₁ | A ₀ | Reg. |
|-----------------|----------------|----------------|------------------|
| 0 | 0 | 0 | Counter 0 |
| 0 | 0 | 1 | Counter 1 |
| 0 | 1 | 0 | Counter 2 |
| 0 | 1 | 1 | Control Register |

P.T.O

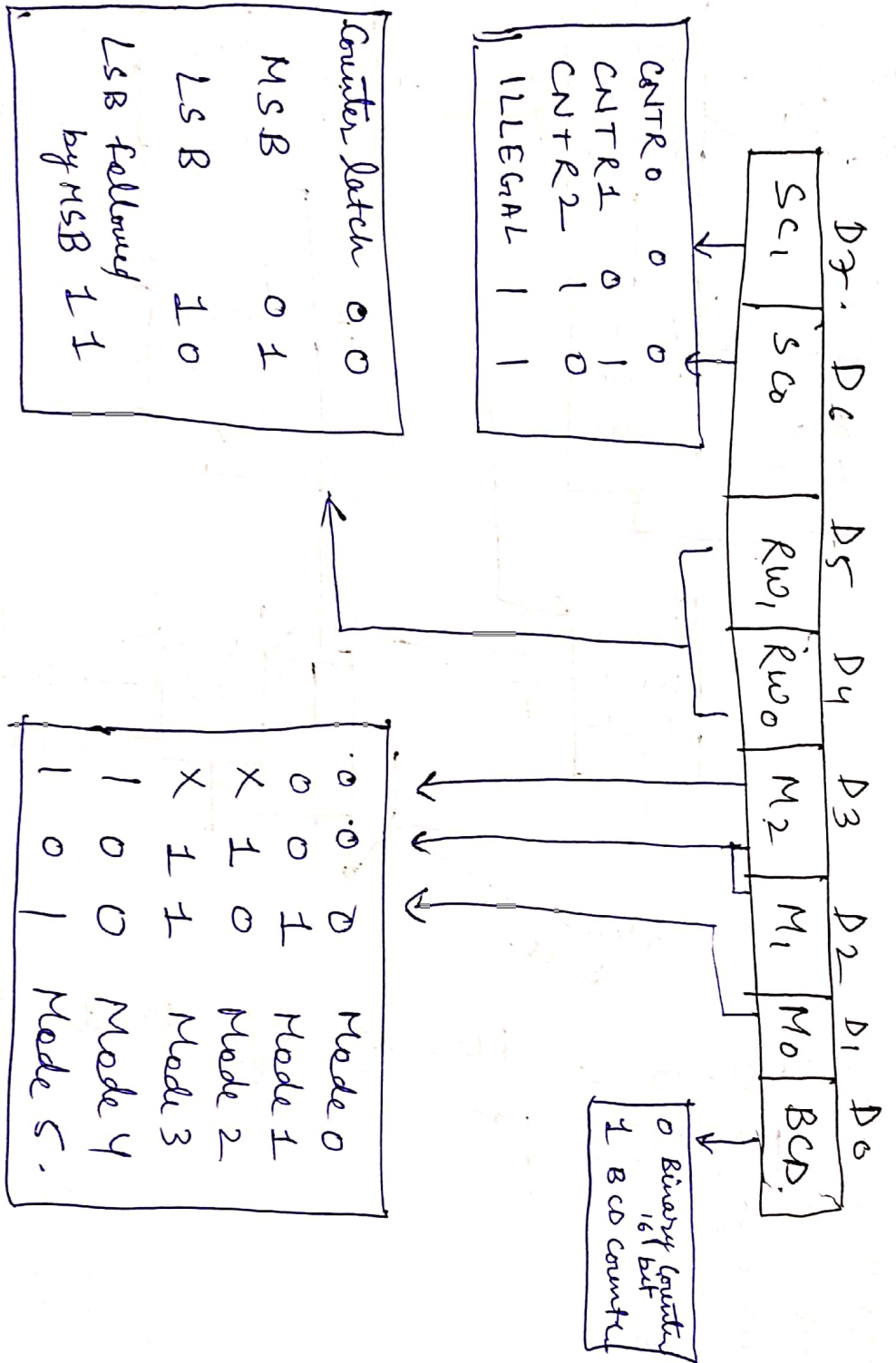


Mode 0: - Interrupt on terminal Count.

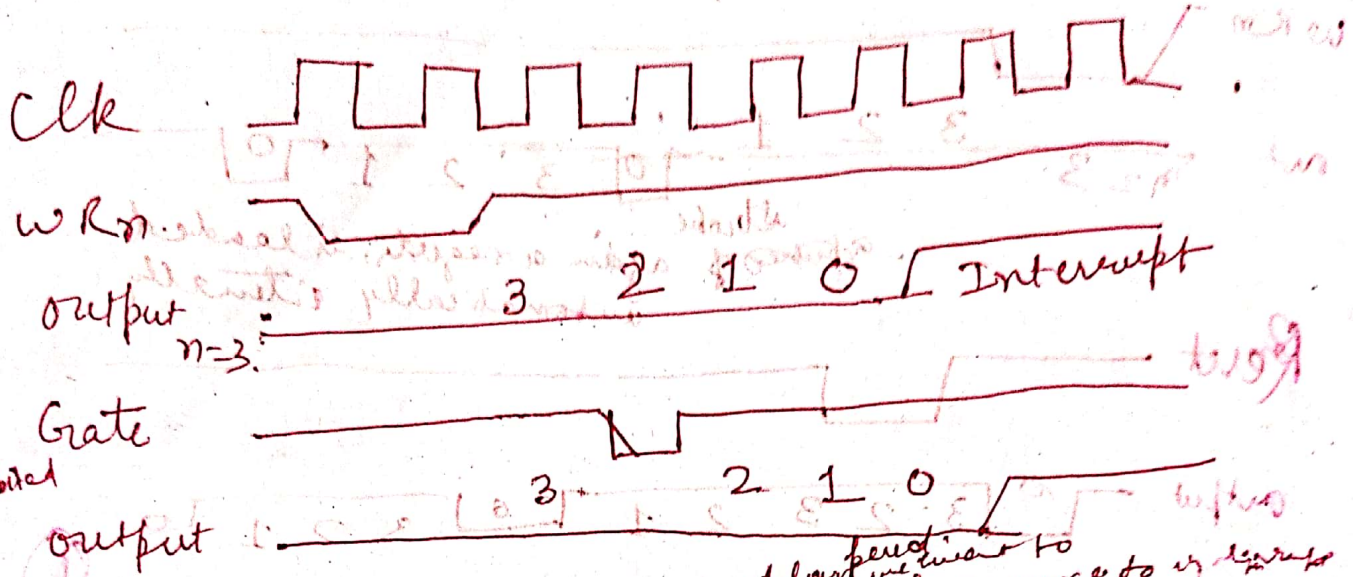

Application :- to generate ^{delay period} ~~microprocessor~~ ^{microprocessor} to ~~in~~ ⁱⁿ ~~sequence~~ ^{sequence}




Mode 1: Hardware Retriggerable one-shot

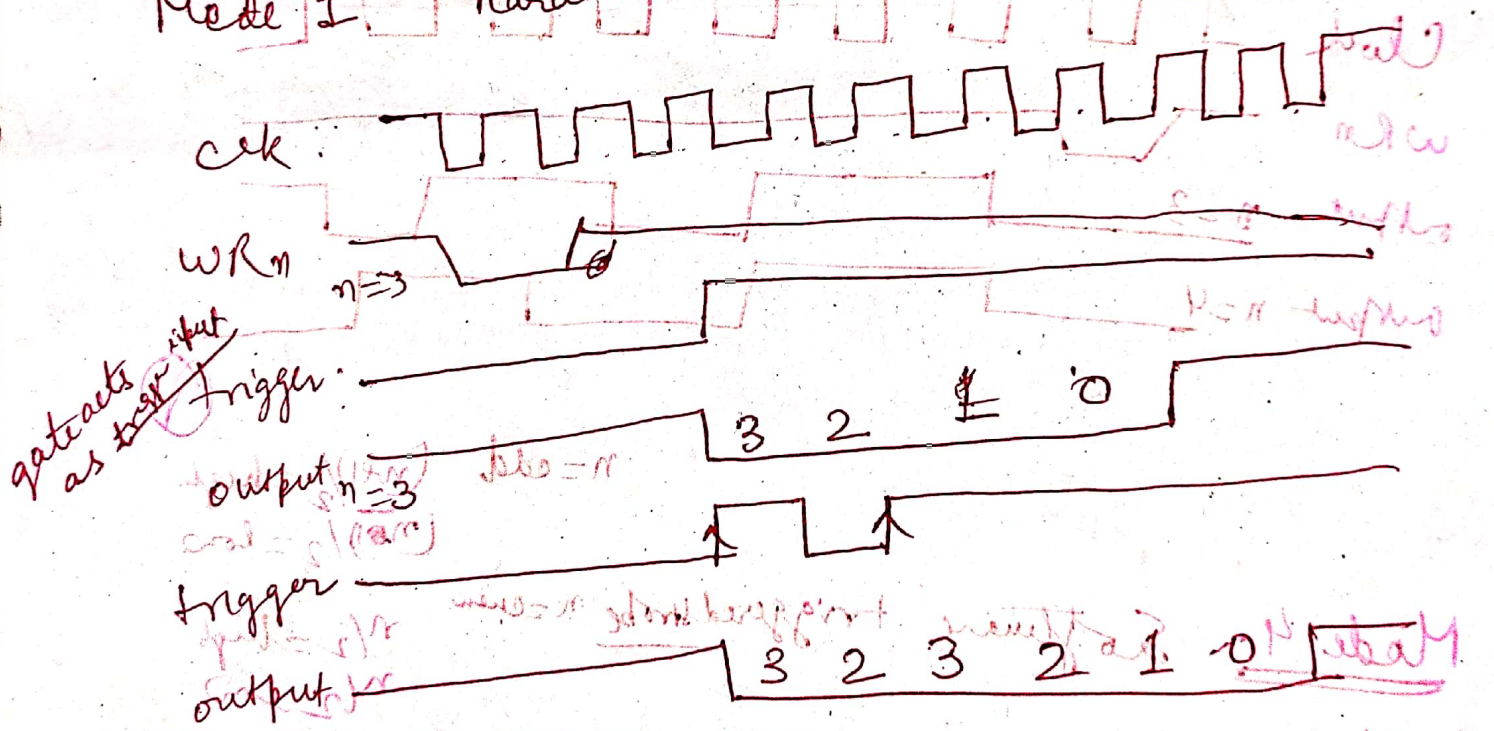

Retriggerable mode

①

Mode 2 Rate generator

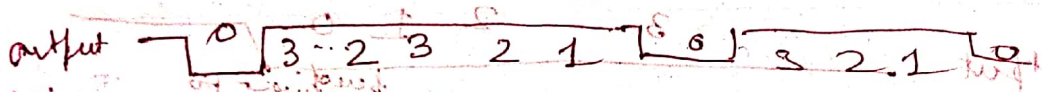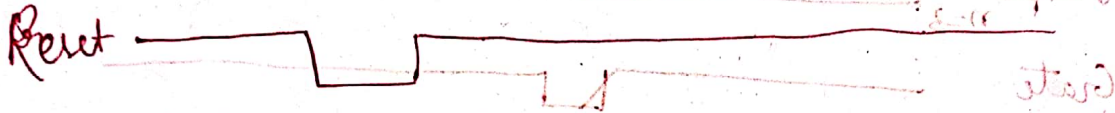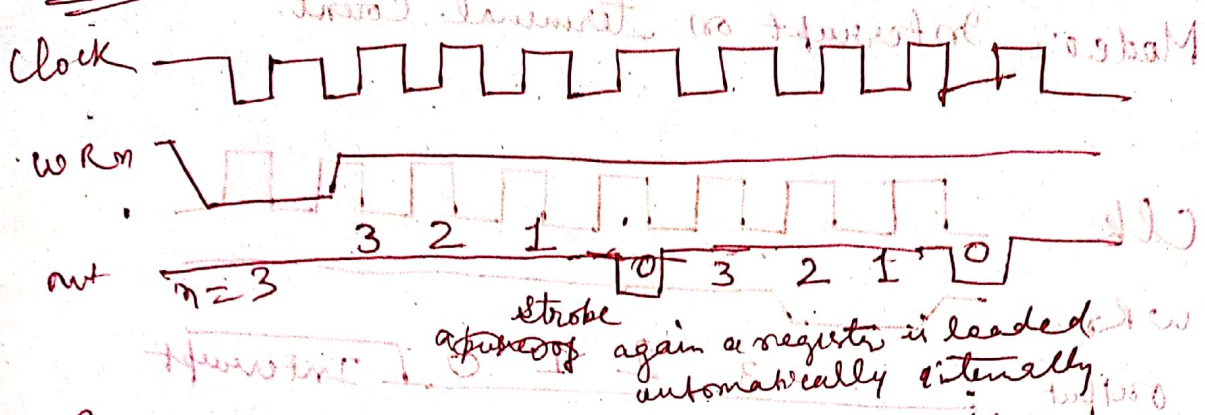


Mode 3 Square wave generator




$n = \text{odd} \quad \frac{(n+1)}{2} = \text{high}$
 $\frac{(n-1)}{2} = \text{low}$

Mode 4 Software triggered strobe n even

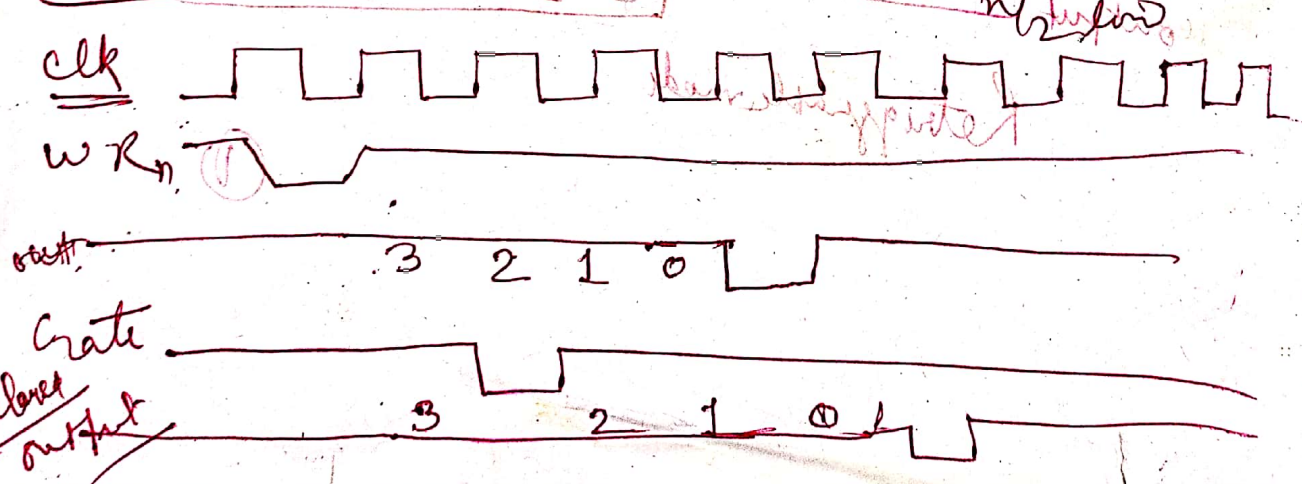

Mode 5 Hardware triggered strobe.

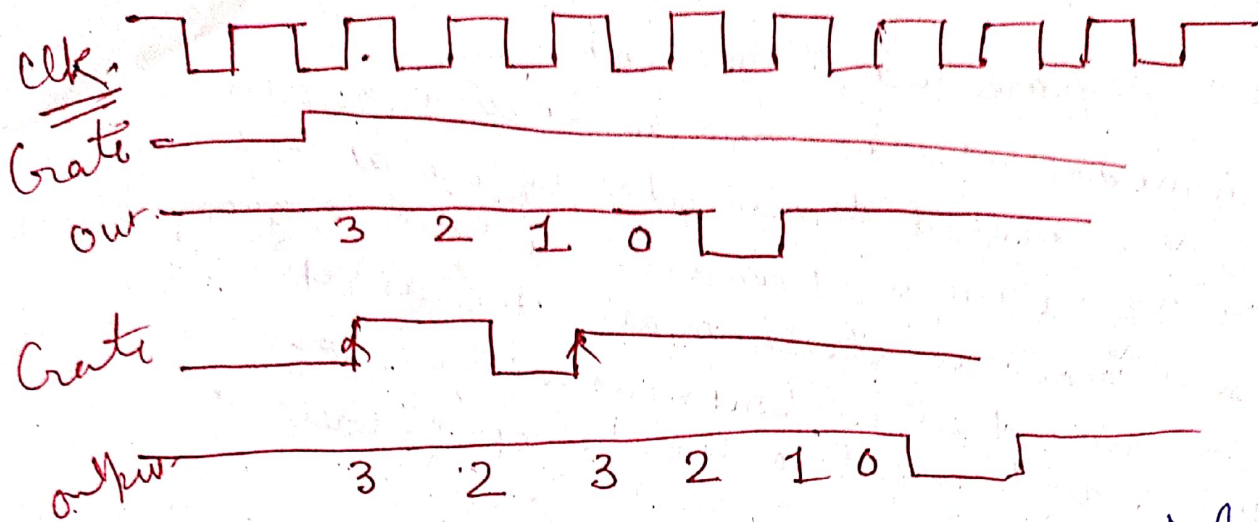

Mode 0 → In this mode, initially the OUT is low. Once a count is loaded in the register, the counter is decremented every cycle, & when ~~the~~ count reaches zero, the out goes high. This can be used as an interrupt. The OUT remains high until a new count or command word is loaded. Fig. also shows that the count is temporarily stopped when the gate is disabled & continues when the gate is at logic 1.

Mode 1 In this mode OUT is initially high. When the gate is triggered OUT goes low and at the end of count OUT goes high again, thus generating a one shot pulse.

Mode 2 This mode is used to generate a pulse equal to the clock period at a given interval. When a count is loaded, the out stays high until the count reaches 1 & out goes low for one clock period. The count is reloaded automatically. The pulse is generated continuously, the count 1 is illegal in this mode.

Mode 3 Square wave generator
In this mode when a count is loaded, the out is high, the count is decremented by two at every clock cycle & when it reaches zero, the out goes low & the count is reloaded again. This is repeated continuously thus a continuous square wave with period equal to the period of count is generated.

Mode 4 → In this mode the out is initially high it goes low for one clock period at the end of the count, the count must be reloaded for subsequent outputs.

Mode 5 This mode is similar to Mode 4, except that it is triggered by rising pulse at the gate. Initially, out is low & when the gate pulse is triggered from low to high, the count begins, at the end of count, the out goes low for one clock period.

